
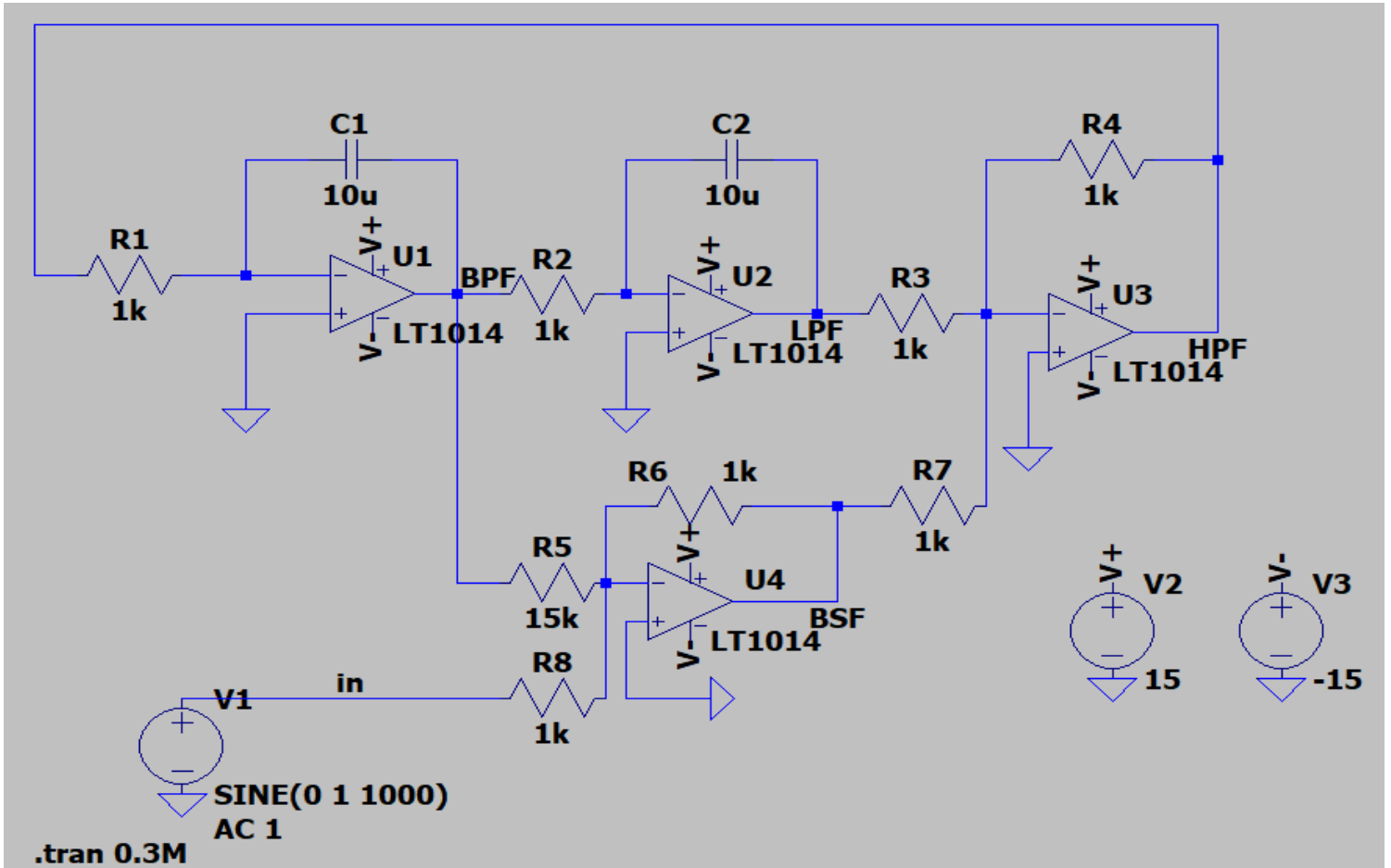


Laboratory 5 work

Design of Analog Filters

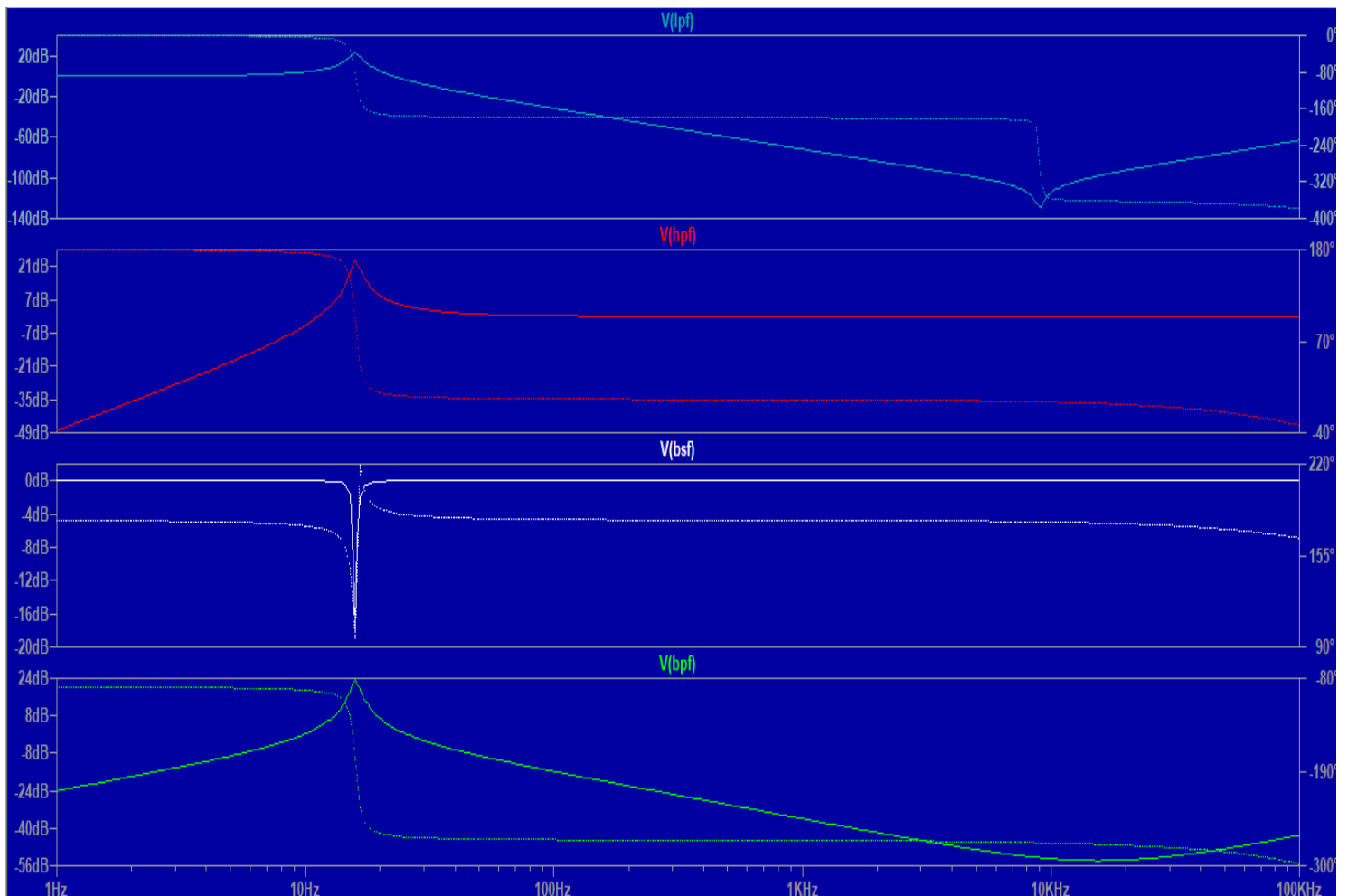


Frequency Response




FFT analysis of filters


Band Pass Filter

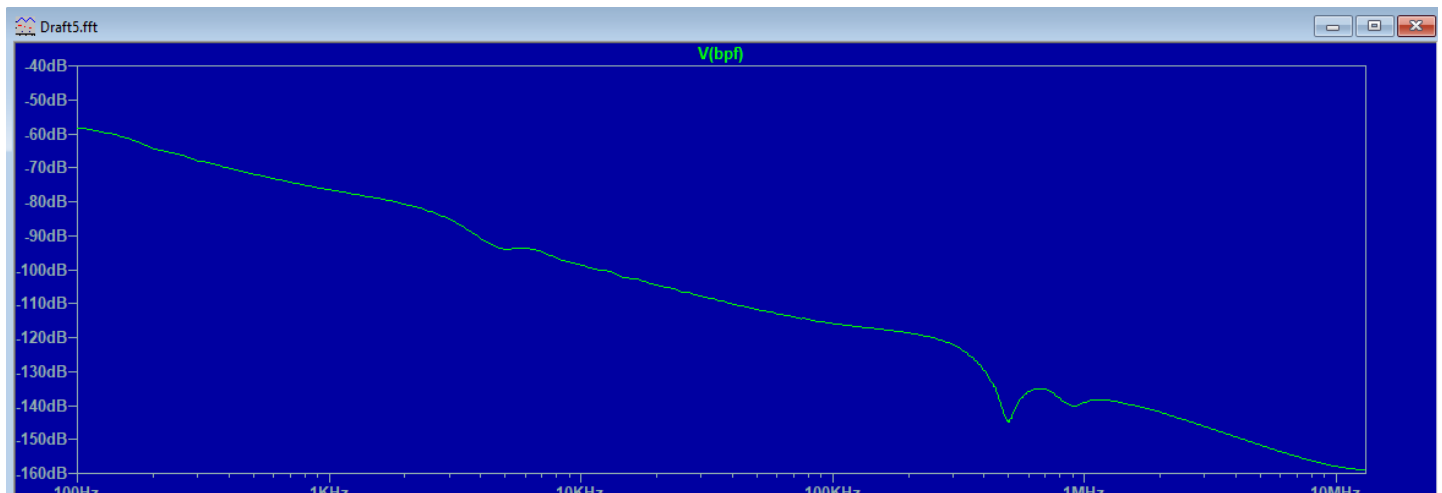

Band Stop Filter

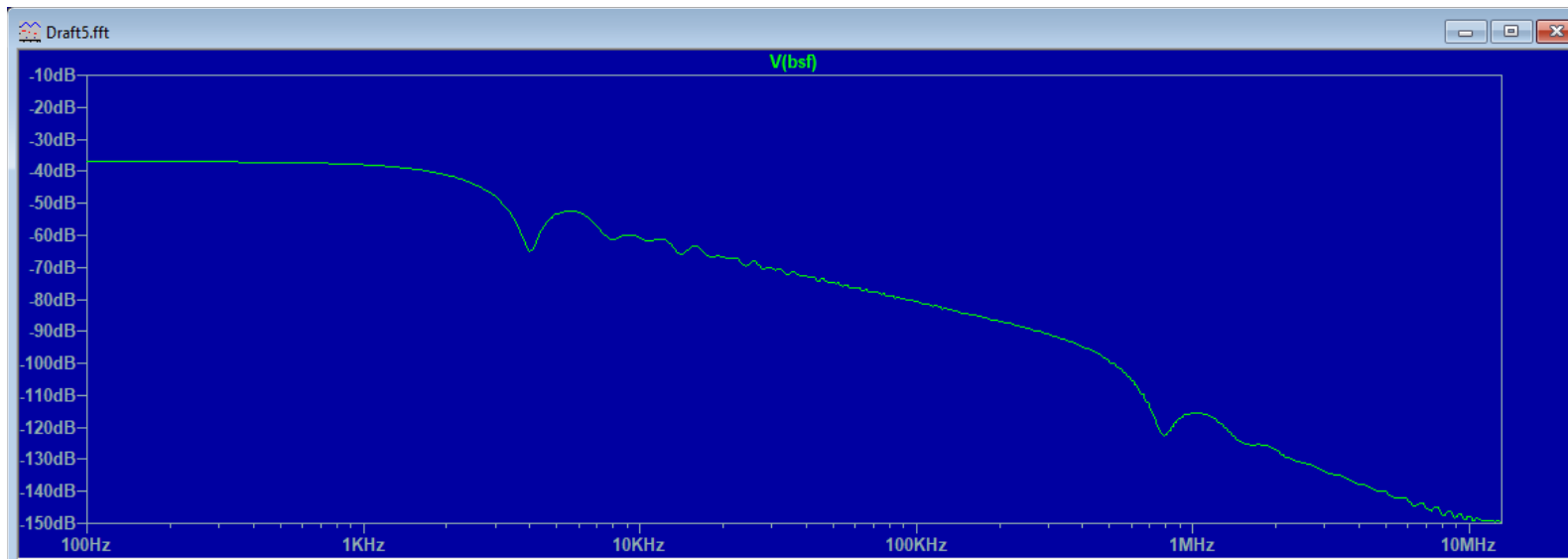

High Pass Filter

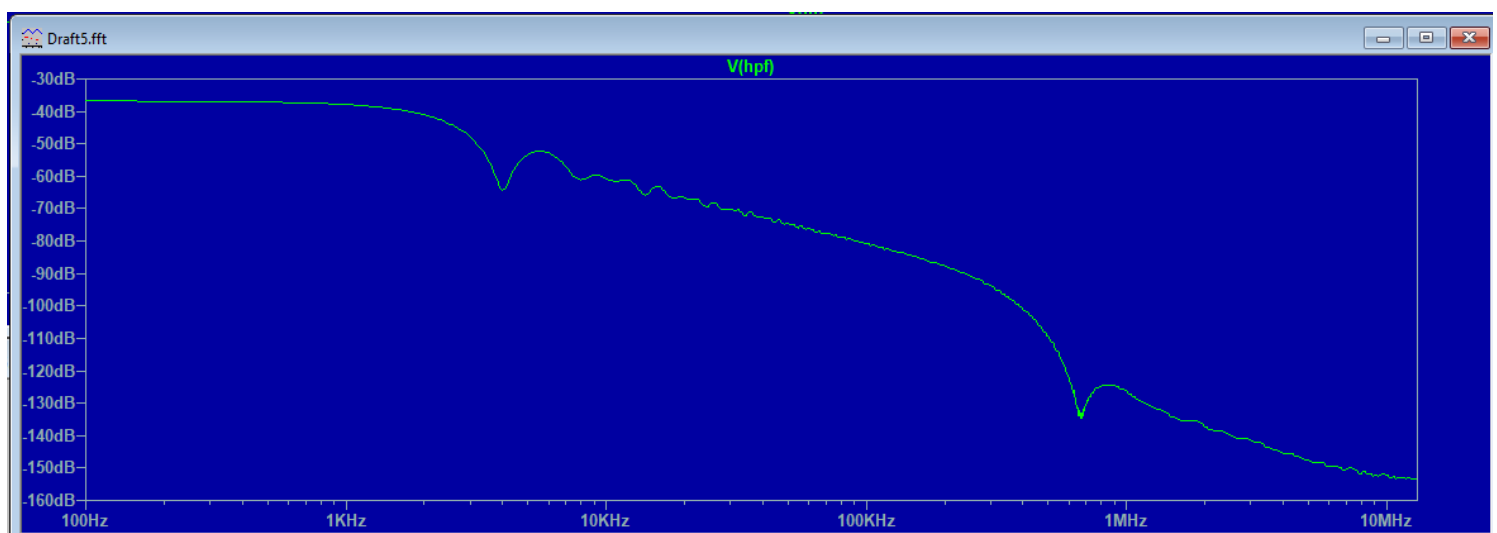

Low Pass Filter

