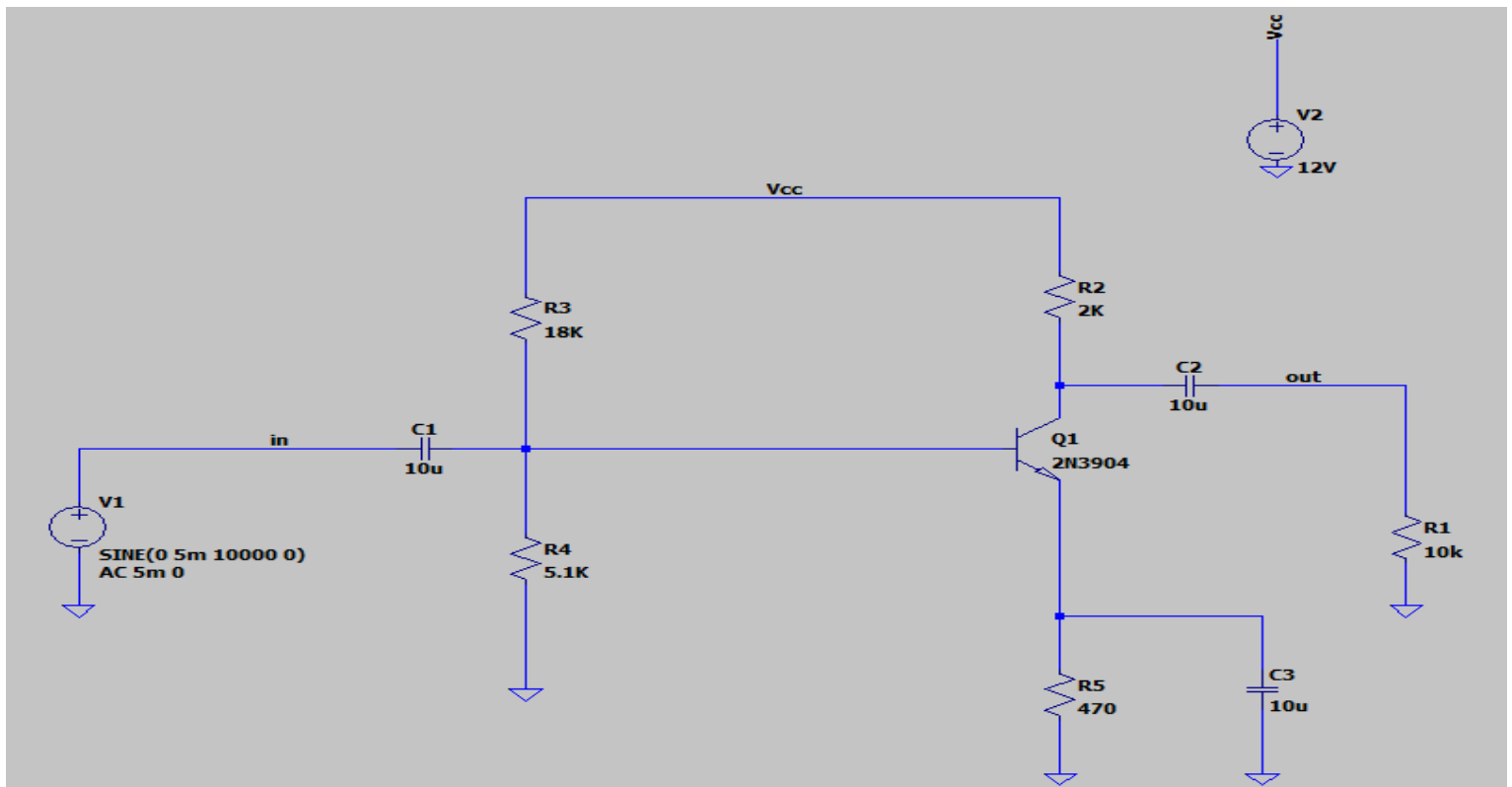


## 2 laboratory work


### Negative feedback in amplifier (modelling with LTspice)


**Work aim:** During laboratory work you will investigate negative feedback (NF) in amplifier and learn how it influences parameters of amplifier.

**Fig. 1.** Amplifier without NF



### AC RESPONSE

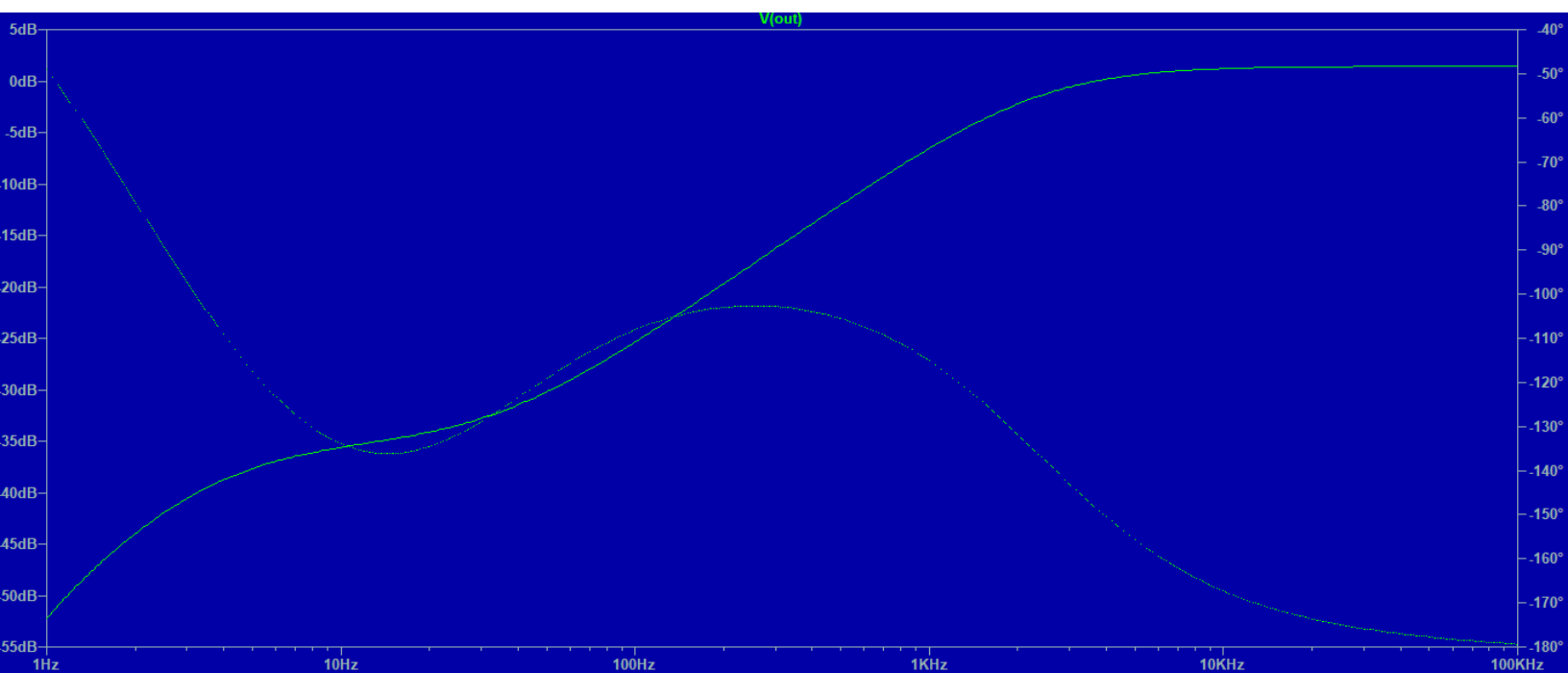

 Draft1.raw
 ✕

Cursor 1

V(out)

Freq: 1.7227928KHz

Mag: -3.0193554dB

Phase: -127.76995°

Group Delay: 42.816273us

Cursor 2

Freq: -- N/A --

Mag: -- N/A --

Phase: -- N/A --

Group Delay: -- N/A --

Ratio (Cursor2 / Cursor1)

Freq: -- N/A --

Mag: -- N/A --

Phase: -- N/A --

Group Delay: -- N/A --

Direct Newton iteration for .op point succeeded.

N-Period=1

Fourier components of V(out)

DC component:0.00575388

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+4	1.141e+0	1.000e+0
2	2.000e+4	4.279e-2	3.751e-2
3	3.000e+4	1.088e-3	9.543e-4
4	4.000e+4	3.785e-4	3.319e-4
5	5.000e+4	8.776e-4	7.694e-4
6	6.000e+4	9.783e-4	8.577e-4
7	7.000e+4	6.661e-4	5.840e-4
8	8.000e+4	3.178e-4	2.786e-4
9	9.000e+4	9.770e-5	8.566e-5

Total Harmonic Distortion: 3.754777%(3.756457%)

Date: Wed May 13 16:08:55 2020


Total elapsed time: 0.089 seconds.

tnom = 27

temp = 27

method = modified trap

totiter = 2107

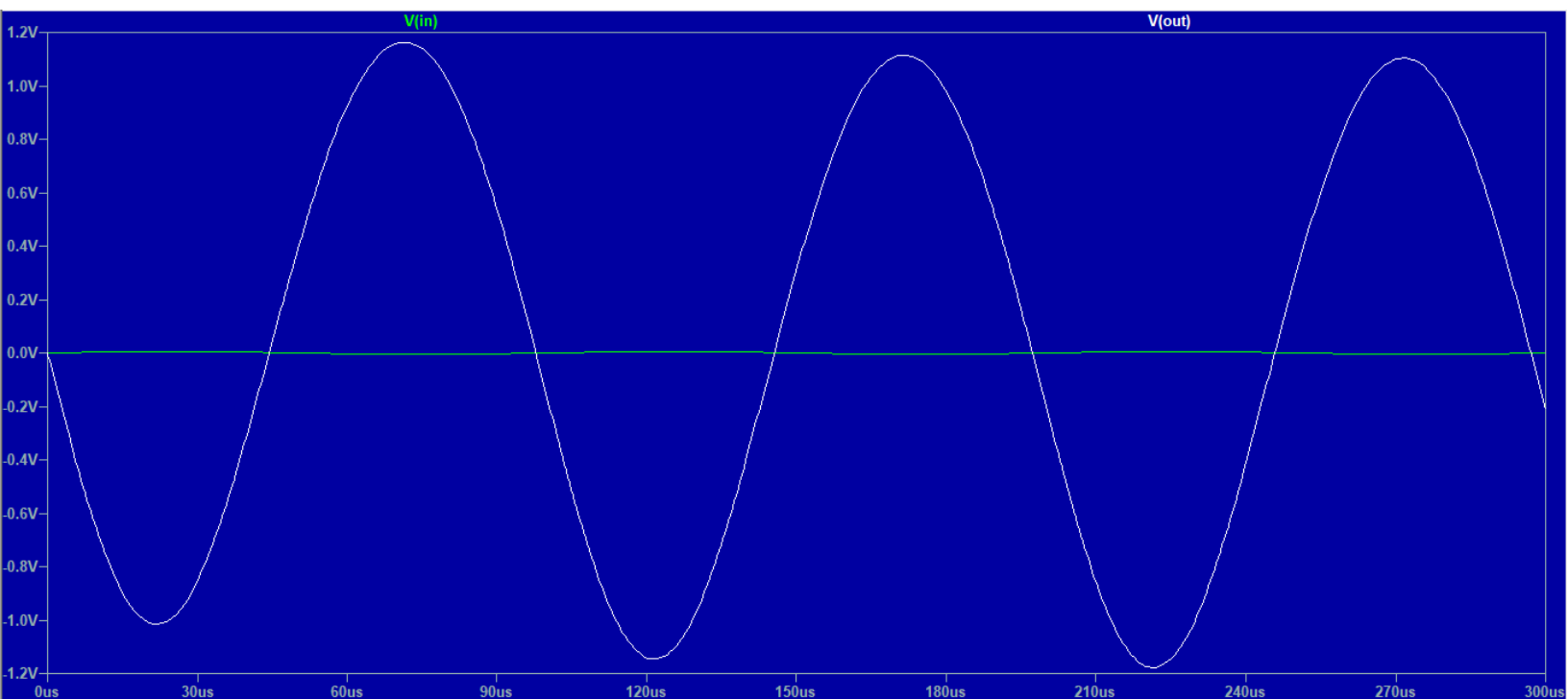

$$71.264368\mu\text{s} - 25.306748\mu\text{s} = 45.95762$$

$$\Phi = (45.95762 / 100.07669\mu\text{s}) \cdot 360^\circ = 165.3206476$$

**Amplifier Input Resistance**

$$U_1 = 5 \times 10^{-3} \text{ V}$$

$$U_2 = 628.51516 \times 10^{-6} \text{ V}$$

$$I_{in} = \frac{U_1 - U_2}{R}$$

$$U_1 - U_2 = R \cdot I_{in}$$

$$Z_{in} = R_{in} = \frac{U_2}{I_{in}} = \frac{R \cdot U_2}{U_1 - U_2} = \frac{R}{U_1 / U_2 - 1}$$

$$\frac{10 \times 10^3 \Omega}{\frac{5 \times 10^{-3}}{628.51516 \times 10^{-6}} - 1} = 1,437.7612710651 R_{in}$$

## Amplifier Output Impedance

U is voltage which is measured when S is OFF and load is not connected

$$\Delta U = U - U_R \quad Z_{out} = \frac{\Delta U}{I} = \frac{U - U_R}{I} = \frac{R(U - U_R)}{U}$$

$$U = 1.3251121 \text{ V}$$


$$R = 10 \text{ K}$$

$$U_R = 1.1151184 \text{ V}$$


$$R(U - U_R) / U = Z_{out}$$

$$\frac{10 \times 10^3 (1.3251121 - 1.1151184)}{1.3251121} = 1,584.7240395737$$

**Fig. 2. Amplifier with current-series NF**

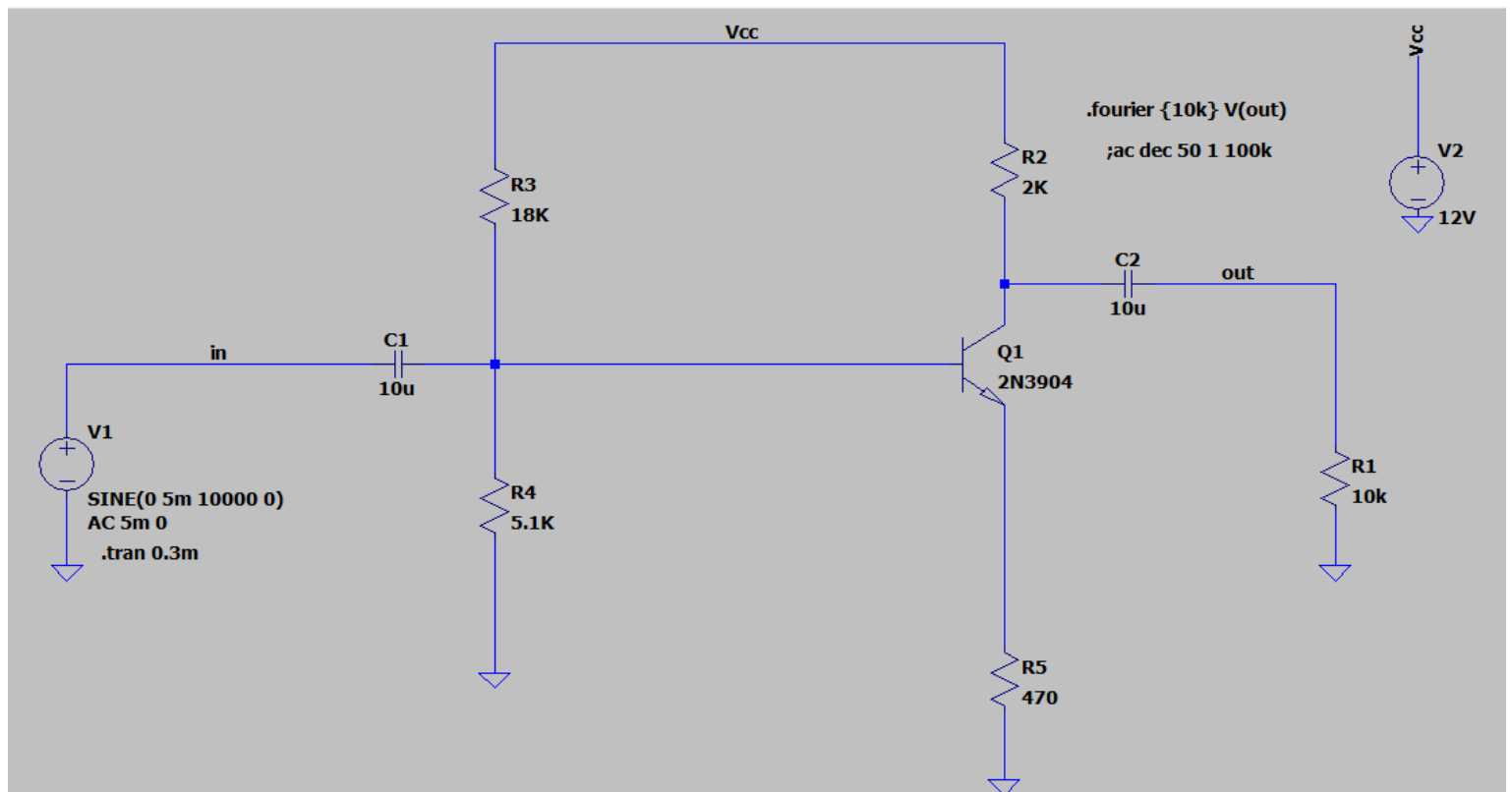

## AC Response and Bandwidth

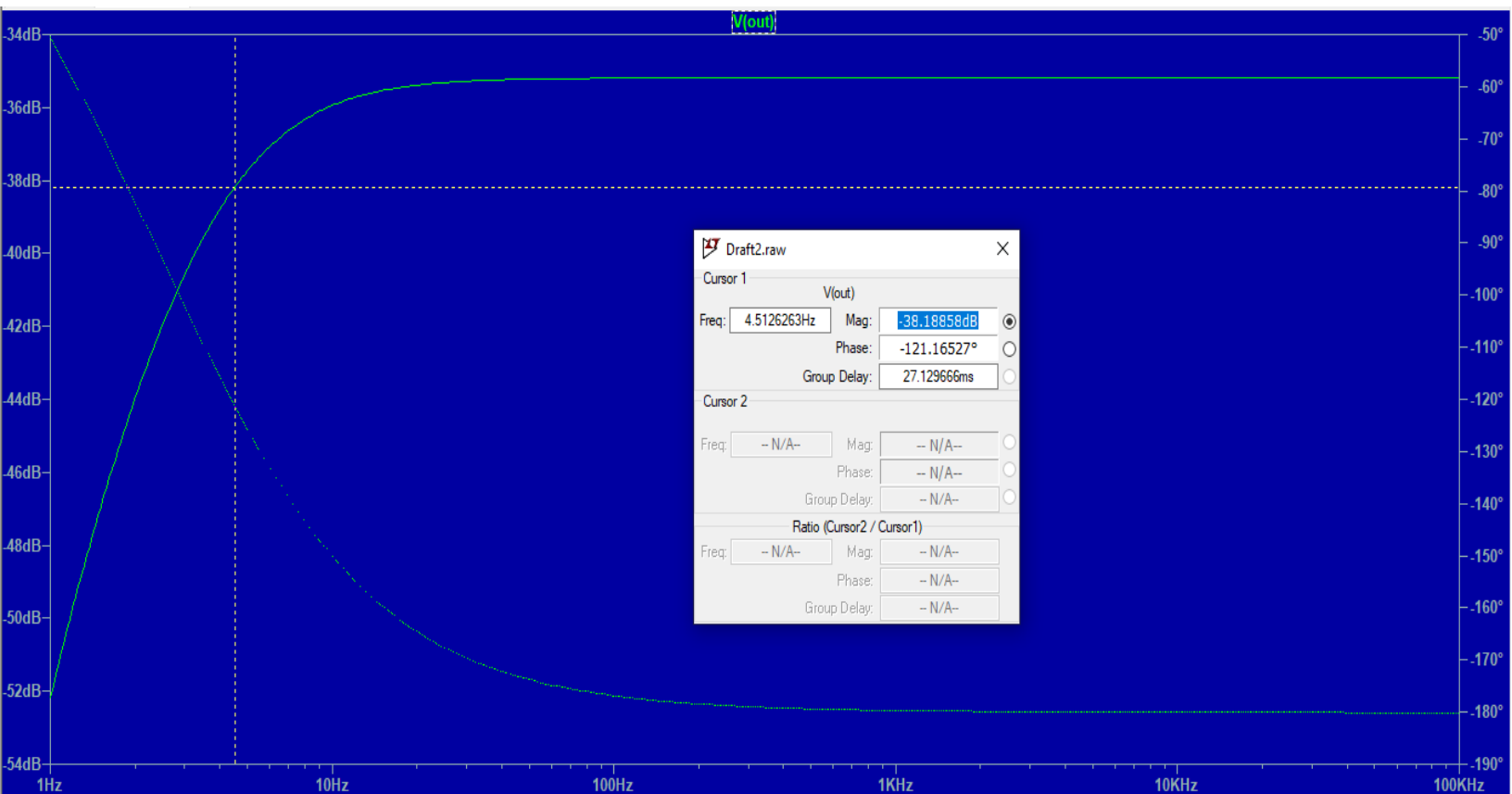

```

SPICE Error Log: C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\2\Draft2.log
Circuit: * C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\2\Draft2.asc
Direct Newton iteration for .op point succeeded.
N-Period=1
Fourier components of V(out)
DC component:-1.35685e-06


Harmonic      Frequency      Fourier      Normalized
Number        [Hz]          Component    Component
  1          1.000e+4      1.740e-2     1.000e+0
  2          2.000e+4      7.577e-6     4.355e-4
  3          3.000e+4      8.813e-6     5.065e-4
  4          4.000e+4      1.185e-5     6.808e-4
  5          5.000e+4      7.785e-6     4.474e-4
  6          6.000e+4      4.515e-6     2.595e-4
  7          7.000e+4      8.387e-6     4.821e-4
  8          8.000e+4      9.804e-6     5.635e-4
  9          9.000e+4      7.787e-6     4.476e-4
Total Harmonic Distortion: 0.138833% (0.161176%)

Date: Sat May 16 22:16:00 2020
Total elapsed time: 0.126 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 2089

```
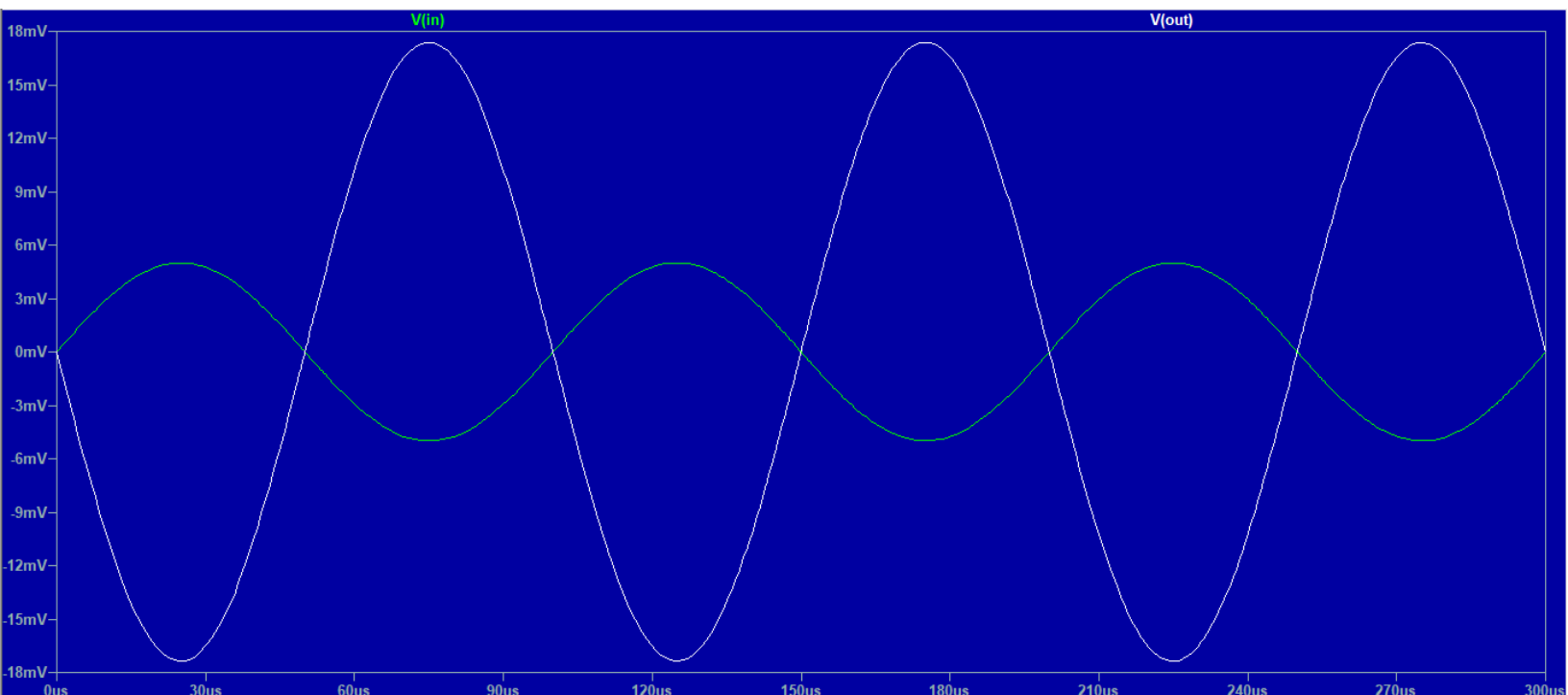
## Phase difference between input and output



$$175.55898\text{us} - 124.90362\text{us} = 50.655336\text{ us}$$

$$\Phi = (50.655336\text{ us} / 100.1542\text{us}) \cdot 360^\circ = 182.079$$

## Amplifier Input Resistance

$$U_1 = 5 \times 10^{-3} \text{ V}$$

$$U_2 = 1.3901944 \times 10^{-3} \text{ V}$$

$$I_{in} = \frac{U_1 - U_2}{R} \quad U_1 - U_2 = R \cdot I_{in} \quad Z_{in} = R_{in} = \frac{U_2}{I_{in}} = \frac{R \cdot U_2}{U_1 - U_2} = \frac{R}{U_1 / U_2 - 1}$$

$$\frac{10 \times 10^3 \Omega}{\frac{5 \times 10^{-3}}{1.3901944 \times 10^{-3}} - 1} = 3,851.1614032623 \text{ R}_{in}$$

## Amplifier Output Impedance

U is voltage which is measured when S is OFF and load is not connected


$$\Delta U = U - U_R \quad Z_{out} = \frac{\Delta U}{I} = \frac{U - U_R}{I} = \frac{R(U - U_R)}{U}$$

$$U = 20.875709 \text{ mV} \quad R = 10 \text{ K} \quad U_R = 17.36763 \text{ mV}$$

$$R(U - U_R) / U = Z_{out}$$


$$\frac{10 \times 10^3 (1.3251121 - 1.1151184)}{1.3251121} = 0.0016804598 \text{ R}$$

**Fig. 3.** Amplifier with voltage-shunt NF

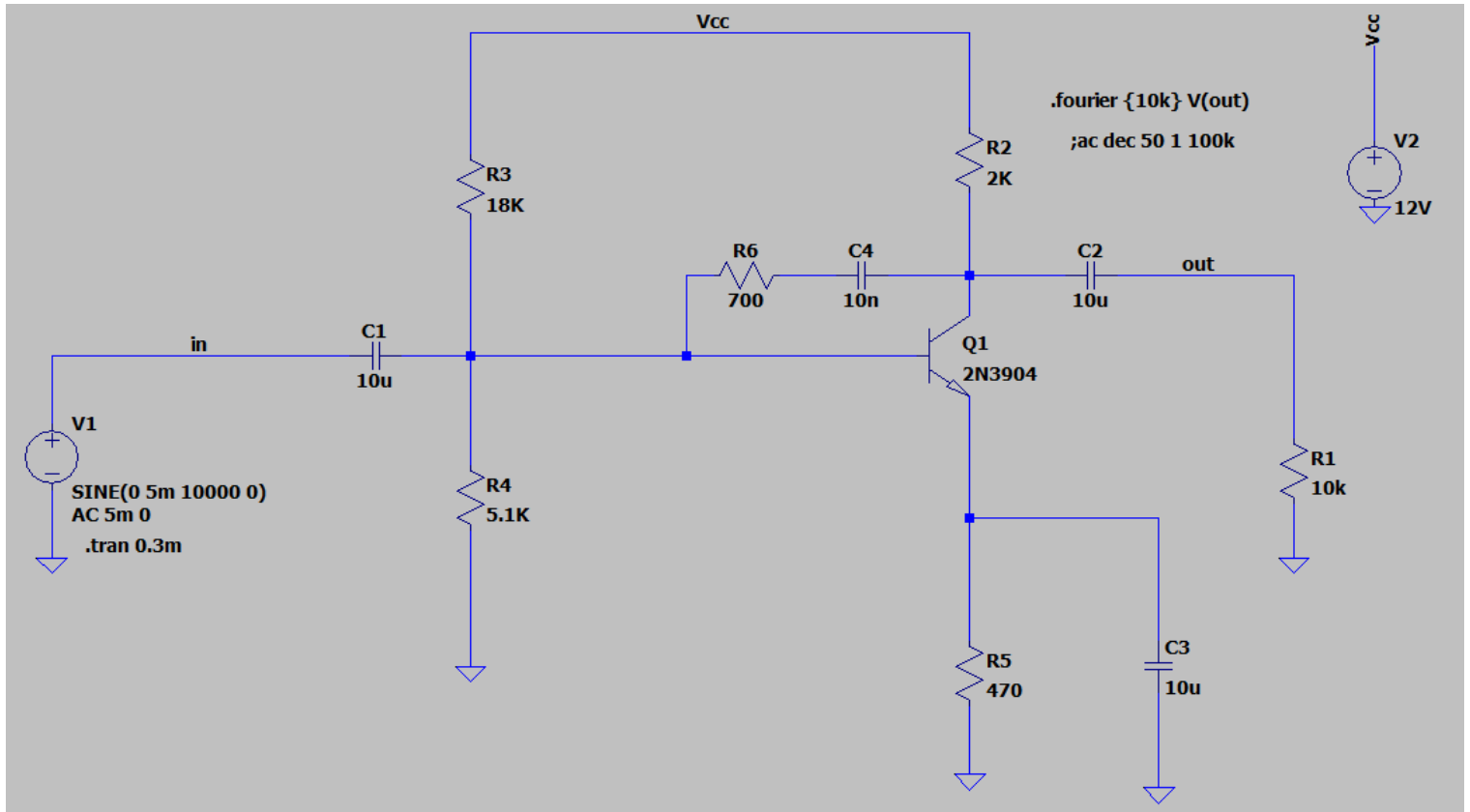

## AC Response and Bandwidth



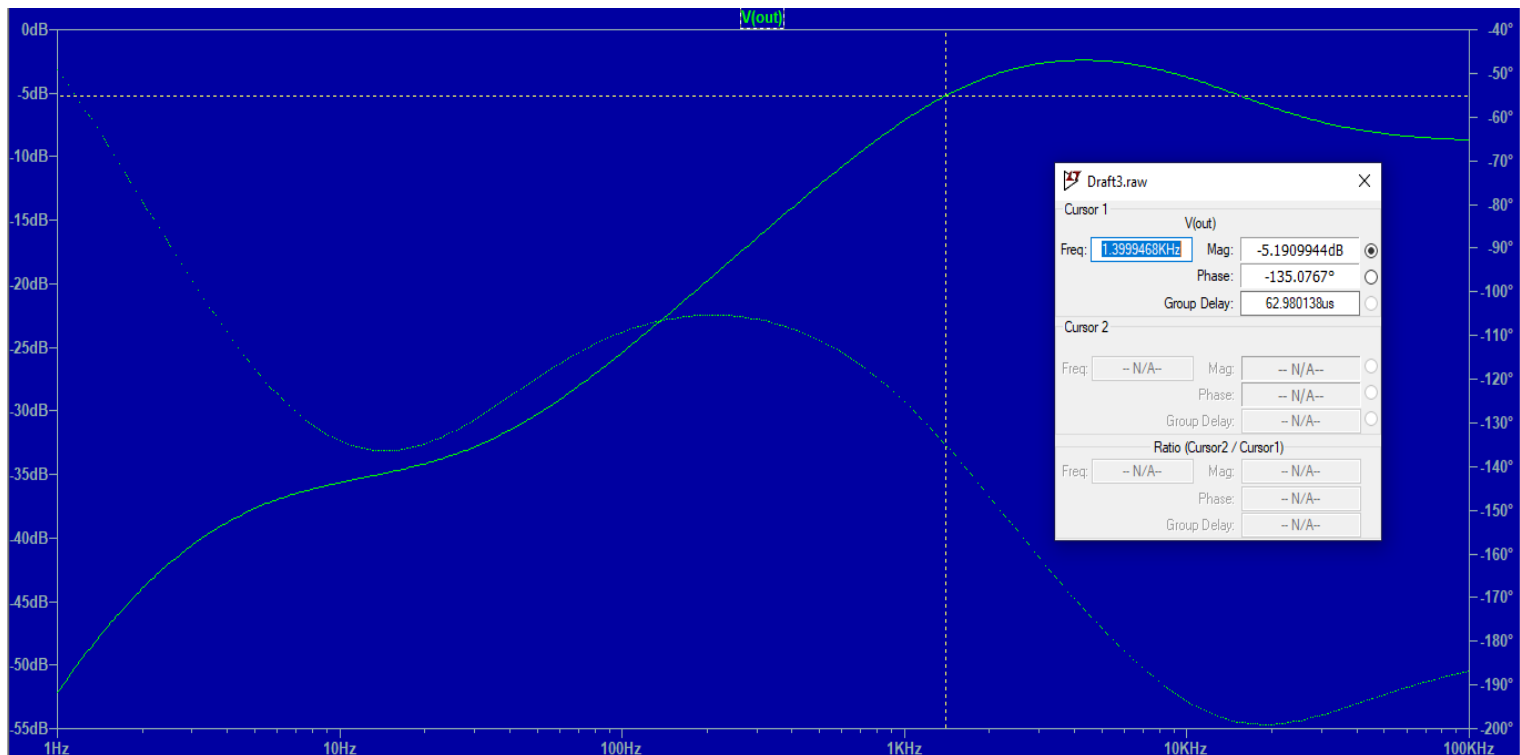

SPICE Error Log: C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\3\Draft3.log

Circuit: \* C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\3\Draft3.asc

Direct Newton iteration for .op point succeeded.

N-Period=1

Fourier components of V(out)

DC component:0.00861999

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+4	6.439e-1	1.000e+0
2	2.000e+4	1.571e-2	2.440e-2
3	3.000e+4	1.093e-3	1.698e-3
4	4.000e+4	7.541e-4	1.171e-3
5	5.000e+4	6.729e-4	1.045e-3
6	6.000e+4	6.205e-4	9.637e-4
7	7.000e+4	4.551e-4	7.068e-4
8	8.000e+4	3.329e-4	5.170e-4
9	9.000e+4	4.068e-4	6.318e-4

Total Harmonic Distortion: 2.455304%(2.460752%)

Date: Sat May 16 22:45:31 2020


Total elapsed time: 0.114 seconds.

tnom = 27

temp = 27

method = modified trap

totiter = 2141

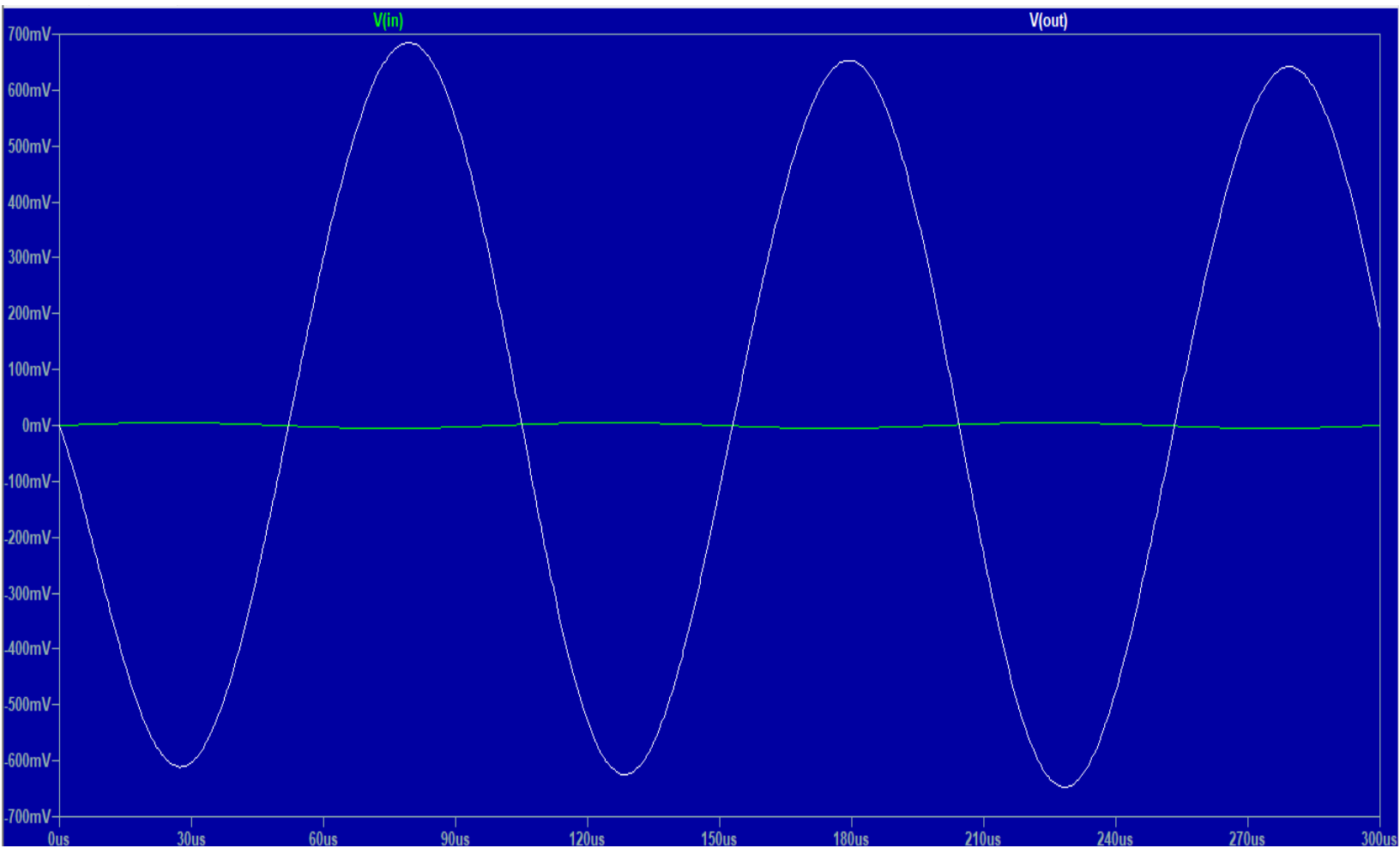

Phase difference between input and output

$$124.46319\mu\text{s} - 79.302326\mu\text{s} = 45.160864$$

$$\Phi = (45.160864 / 105.11628) \cdot 360^\circ = 154.666$$

## Amplifier Input Resistance

$$U_1 = 5 \times 10^{-3} \text{ V}$$

$$U_2 = 29.173455 \times 10^{-6} \text{ V}$$

$$I_{in} = \frac{U_1 - U_2}{R} \quad U_1 - U_2 = R \cdot I_{in} \quad Z_{in} = R_{in} = \frac{U_2}{I_{in}} = \frac{R \cdot U_2}{U_1 - U_2} = \frac{R}{U_1 / U_2 - 1}$$

$$\frac{10 \times 10^3 \Omega}{\frac{5 \times 10^{-3}}{1.3901944 \times 10^{-3}} - 1} = 58.6893441883 R_{in}$$

## Amplifier Output Impedance

U is voltage which is measured when S is OFF and load is not connected


$$\Delta U = U - U_R \quad Z_{out} = \frac{\Delta U}{I} = \frac{U - U_R}{I} = \frac{R(U - U_R)}{U}$$

$$U = 711.007 \text{ mV} \quad R = 10 \text{ K} \quad U_R = 652.99687 \text{ mV}$$


$$R(U - U_R) / U = Z_{out}$$

$$\frac{10 \times 10^3 (1.3251121 - 1.1151184)}{1.3251121} = 815.886904067 \text{ R}$$

**Fig. 4. Amplifier with voltage-series NF**

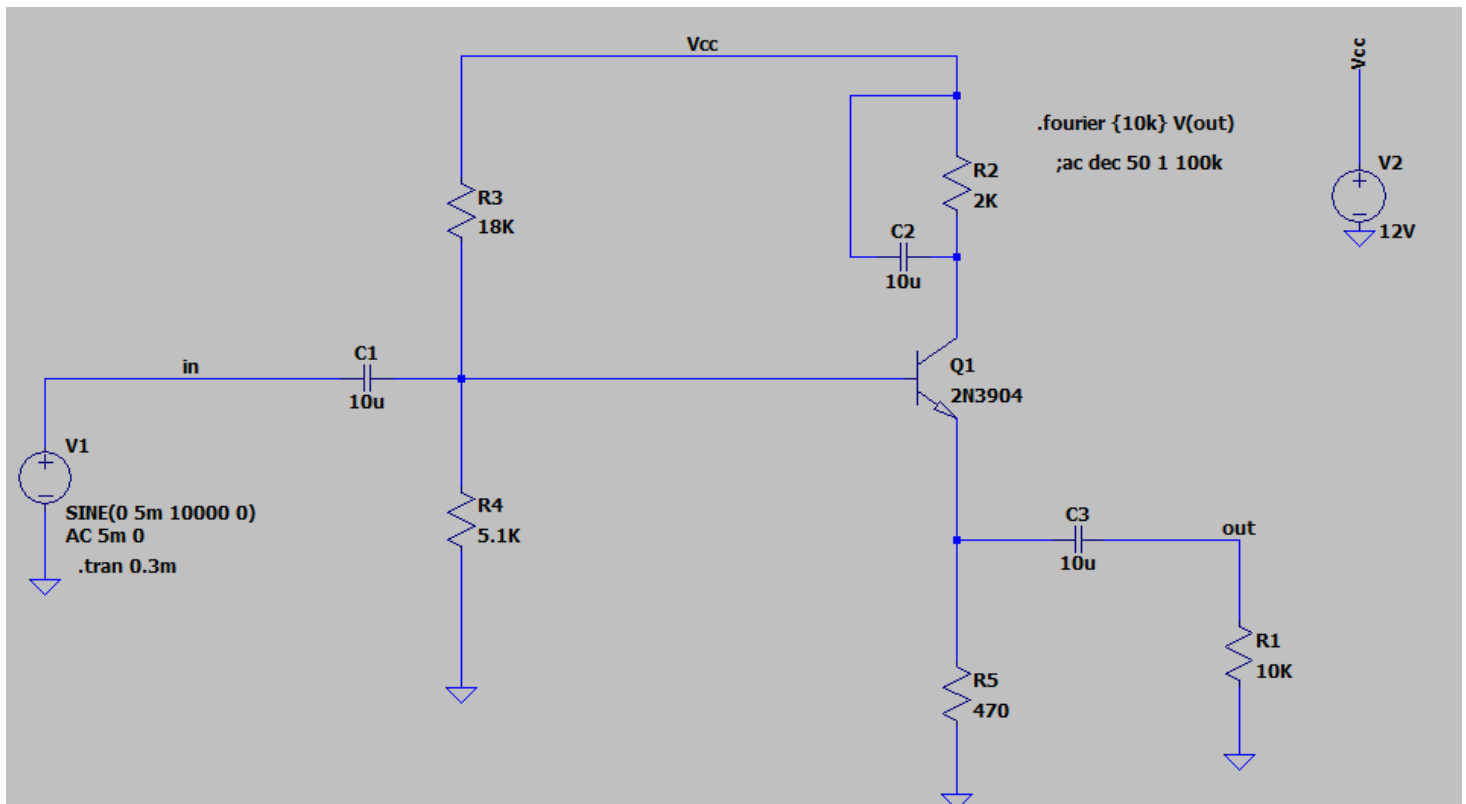

**AC Response**

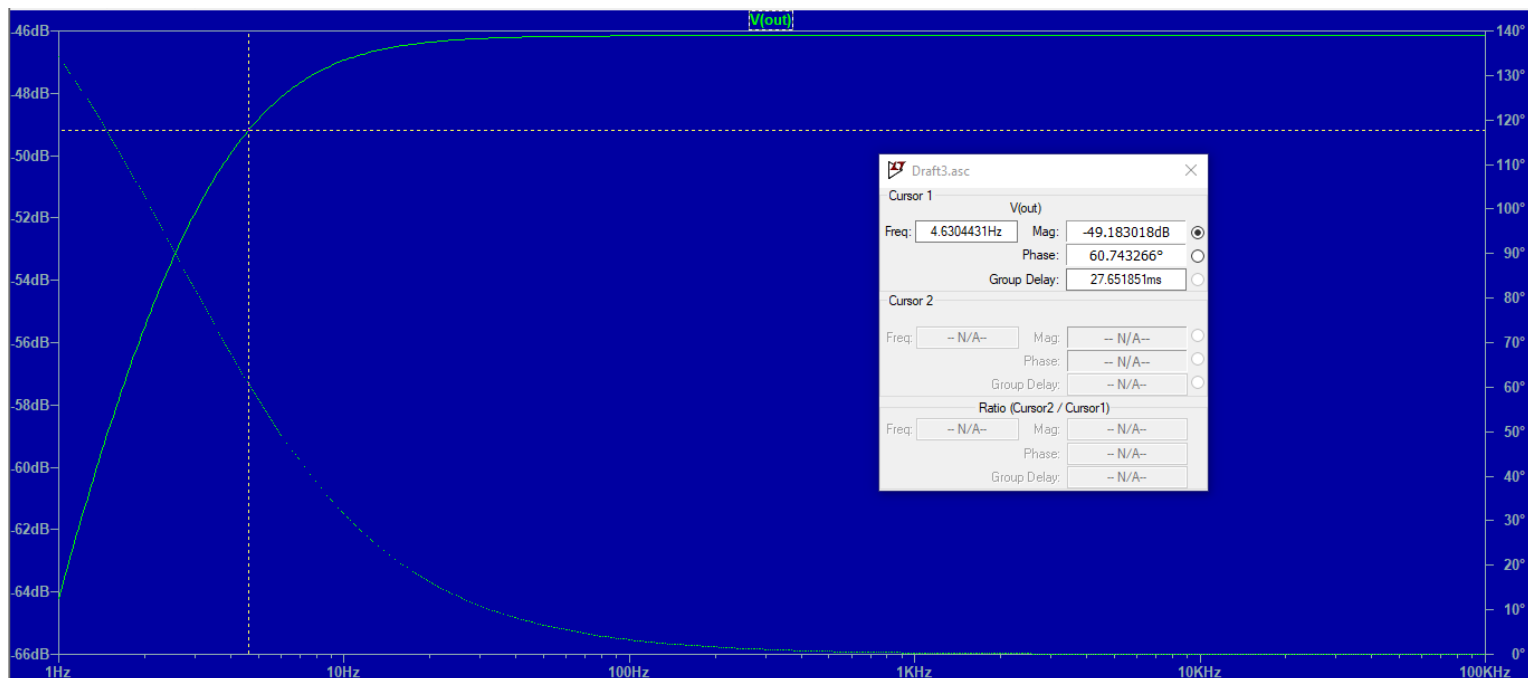

SPICE Error Log: C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\3\Draft3.log

Circuit: \* C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\3\Draft3.asc

Direct Newton iteration for .op point succeeded.

N-Period=1

Fourier components of V(out)

DC component:5.21588e-07

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+4	4.925e-3	1.000e+0
2	2.000e+4	7.472e-7	1.517e-4
3	3.000e+4	3.105e-6	6.303e-4
4	4.000e+4	1.552e-6	3.152e-4
5	5.000e+4	3.021e-6	6.134e-4
6	6.000e+4	1.727e-6	3.506e-4
7	7.000e+4	1.601e-6	3.251e-4
8	8.000e+4	1.110e-6	2.254e-4
9	9.000e+4	1.714e-6	3.480e-4

Total Harmonic Distortion: 0.113862%(0.139162%)

Date: Sun May 17 13:33:26 2020


Total elapsed time: 0.134 seconds.

tnom = 27

temp = 27

method = modified trap

totiter = 2090

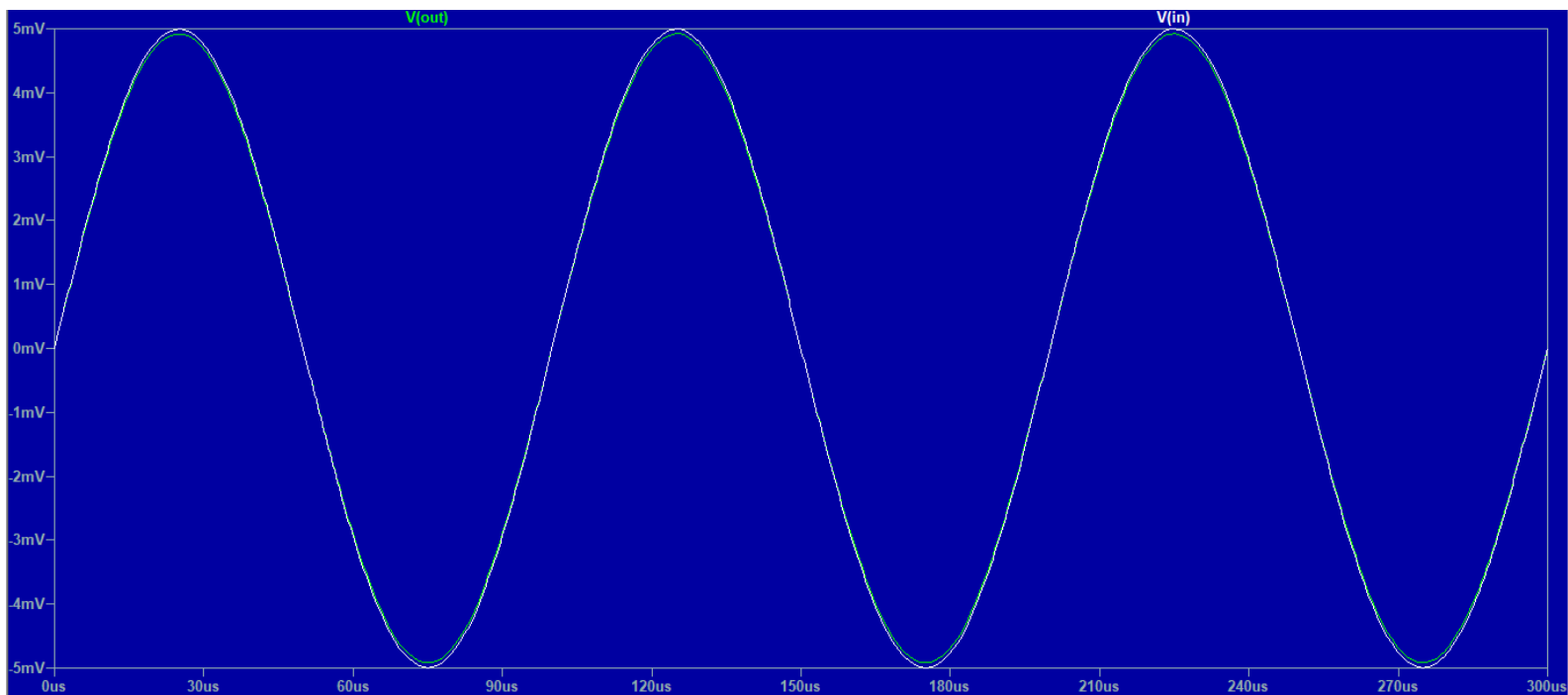

$$25.233645\mu s - 25\mu s = 0.233645$$

$$\Phi = (0.233645 / 100\mu s) \cdot 360 = 0.841$$

## Amplifier Input Resistance

$$U_1 = 5 \times 10^{-3} \text{ V}$$

$$U_2 = 1.389993 \text{ mV}$$

$$I_{in} = \frac{U_1 - U_2}{R} \quad U_1 - U_2 = R \cdot I_{in} \quad Z_{in} = R_{in} = \frac{U_2}{I_{in}} = \frac{R \cdot U_2}{U_1 - U_2} = \frac{R}{U_1 / U_2 - 1}$$

$$\frac{10 \times 10^3 \Omega}{\frac{5 \times 10^{-3}}{1.389993 \times 10^{-3} \text{ V}} - 1} = 3,850.3886557561 R_{in}$$

## Amplifier Output Impedance

U is voltage which is measured when S is OFF and load is not connected


$$\Delta U = U - U_R \quad Z_{out} = \frac{\Delta U}{I} = \frac{U - U_R}{I} = \frac{R(U - U_R)}{U}$$

$$U = 4.9453263 \text{ mV} \quad R = 10 \text{ K} \quad U_R = 4.9257289 \text{ mV}$$

$$R(U - U_R) / U = Z_{out}$$


$$\frac{10 \times 10^3 (4.9453263 \text{ mV} - 4.9257289 \text{ mV})}{4.9453263 \text{ mV}} = 39.628123 R$$

**Fig. 5. Amplifier with current-shunt NF**

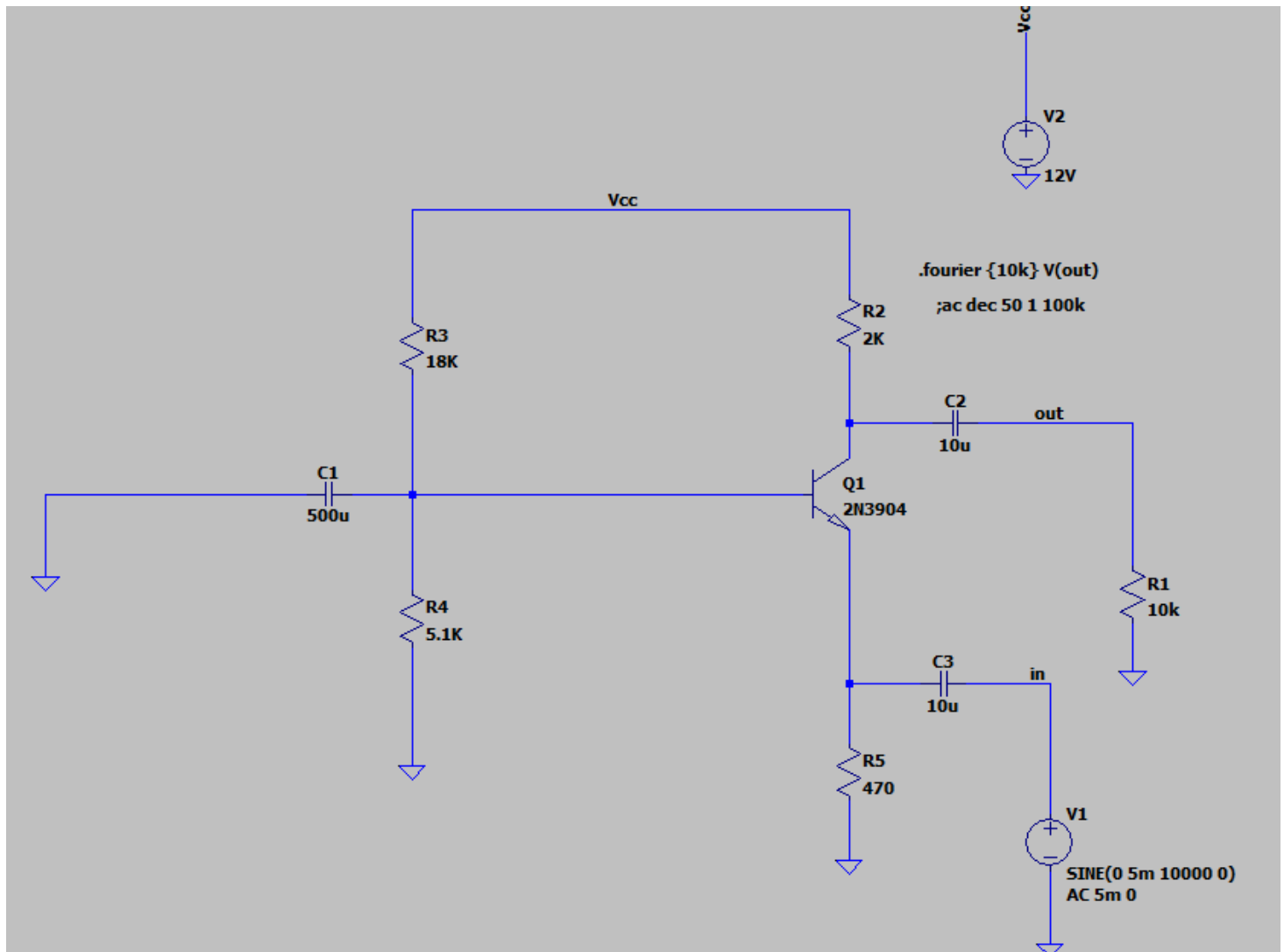



# AC Response and bandwitdh

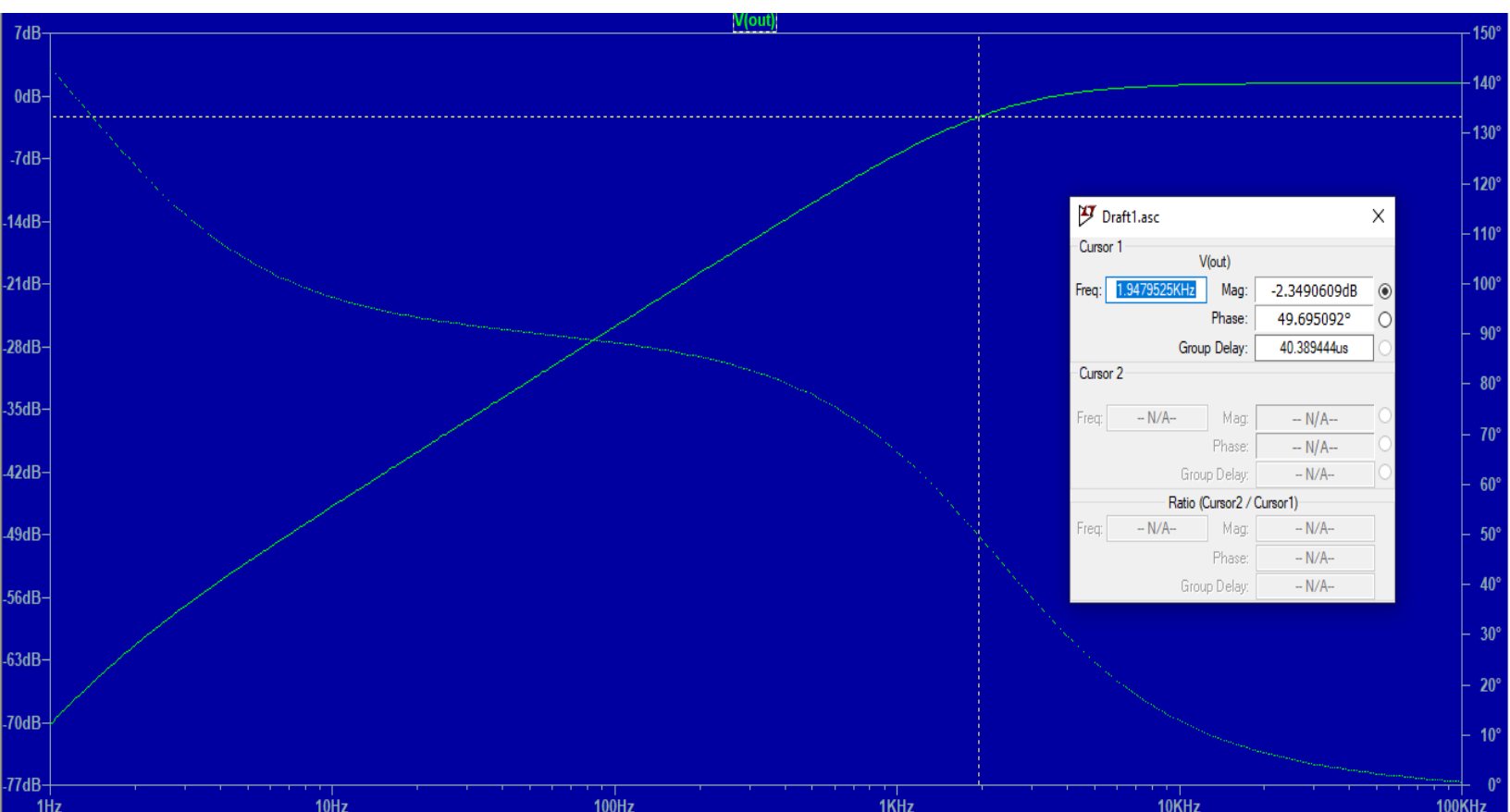

SPICE Error Log: C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\5\Draft1.log

Circuit: \* C:\Users\templ\OneDrive\Masaüstü\lab work 2 anal\5\Draft1.asc


Direct Newton iteration for .op point succeeded.  
N-Period=1  
Fourier components of V(out)  
DC component:-0.00929792

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+4	1.142e+0	1.000e+0
2	2.000e+4	4.421e-2	3.870e-2
3	3.000e+4	1.498e-3	1.311e-3
4	4.000e+4	1.299e-3	1.137e-3
5	5.000e+4	9.073e-4	7.943e-4
6	6.000e+4	2.229e-4	1.951e-4
7	7.000e+4	7.642e-4	6.690e-4
8	8.000e+4	4.032e-4	3.529e-4
9	9.000e+4	3.459e-4	3.028e-4

Total Harmonic Distortion: 3.875656%(3.878008%)

Date: Sun May 17 13:52:54 2020  
Total elapsed time: 0.131 seconds.

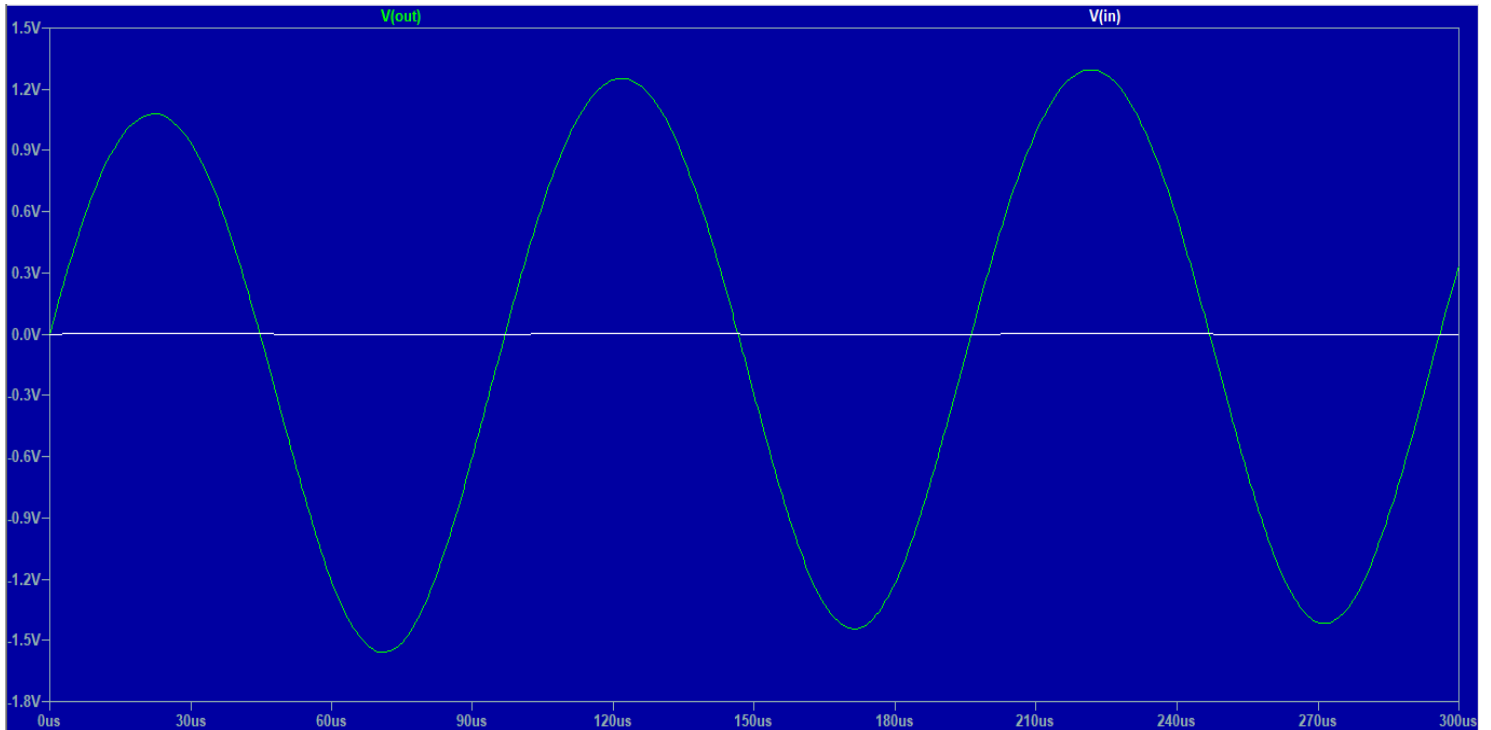tnom = 27  
temp = 27  
method = modified trap  
totiter = 2087



$$25.076687\mu s - 22.758621\mu s = 2.318066$$

$$\Phi = (2.318066 / 96.781609\mu s) \cdot 360^\circ = 8.622544824$$

## Amplifier Input Resistance

$$U_1 = 5 \times 10^{-3} \text{ V}$$

$$U_2 = 7.640542 \mu\text{V}$$

$$I_{in} = \frac{U_1 - U_2}{R} \quad U_1 - U_2 = R \cdot I_{in} \quad Z_{in} = R_{in} = \frac{U_2}{I_{in}} = \frac{R \cdot U_2}{U_1 - U_2} = \frac{R}{U_1 / U_2 - 1}$$

$$\frac{10 \times 10^3 \Omega}{\frac{5 \times 10^{-3}}{7.640542 \mu\text{V}} - 1} = 15.3044708905 R_{in}$$

## Amplifier Output Impedance

U is voltage which is measured when S is OFF and load is not connected

$$\Delta U = U - U_R \quad Z_{out} = \frac{\Delta U}{I} = \frac{U - U_R}{I} = \frac{R(U - U_R)}{U}$$

$$U = 1.2524552 \text{ V} \quad R = 10\text{K} \quad U_R = 1.0555553 \text{ V}$$

$$R(U - U_R) / U = Z_{out}$$

$$\frac{10 \times 10^3 (1.2524552 \text{ V} - 1.0555553)}{1.2524552 \text{ V}} = 1,572.111322 \text{ R}$$

