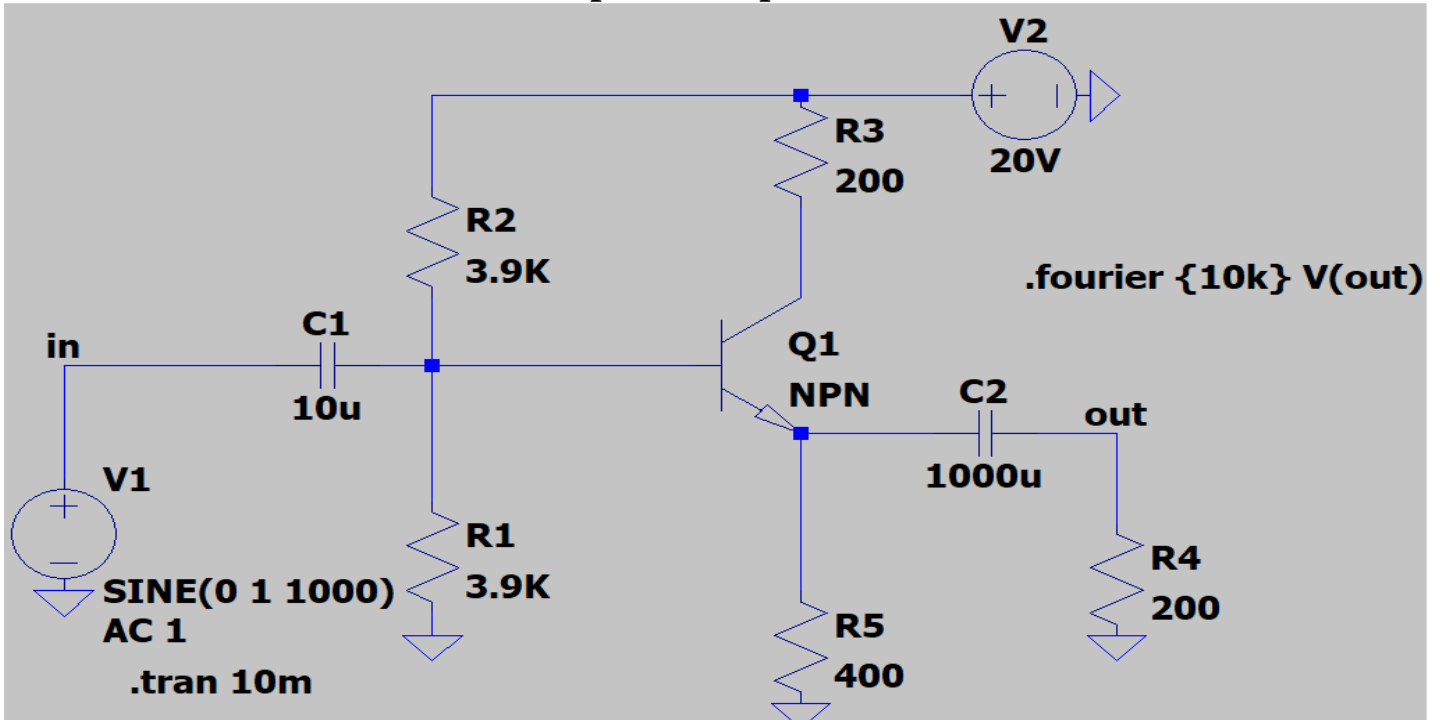


3 laboratory work


Investigation of power amplifier

Work aim: – to learn and understand about transistor power amplifier and its parameters, circuits.


Class A power amplifier



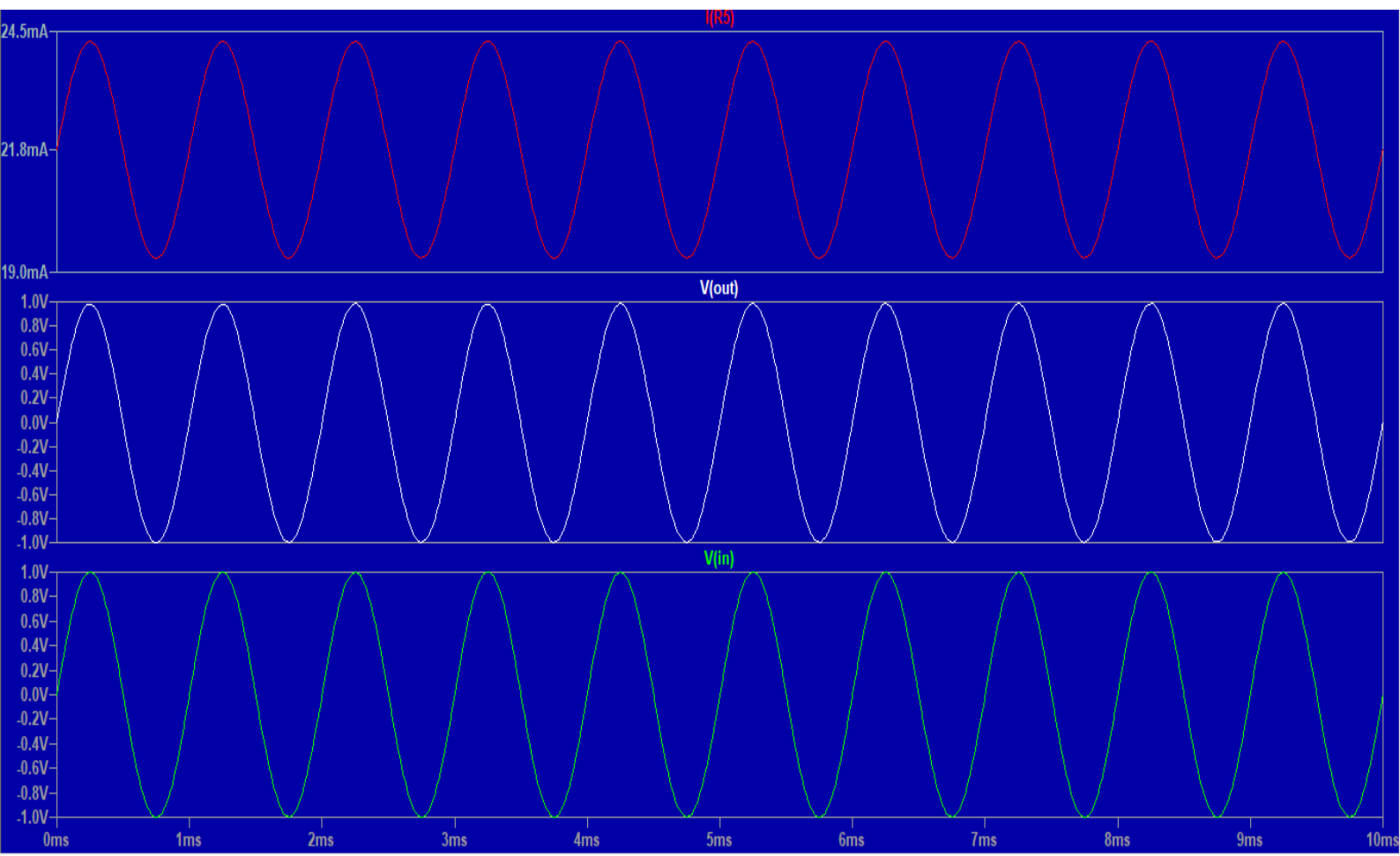Transient Response of input, output, current I_E of Class A power amplifier:



AC Response and Bandwidth

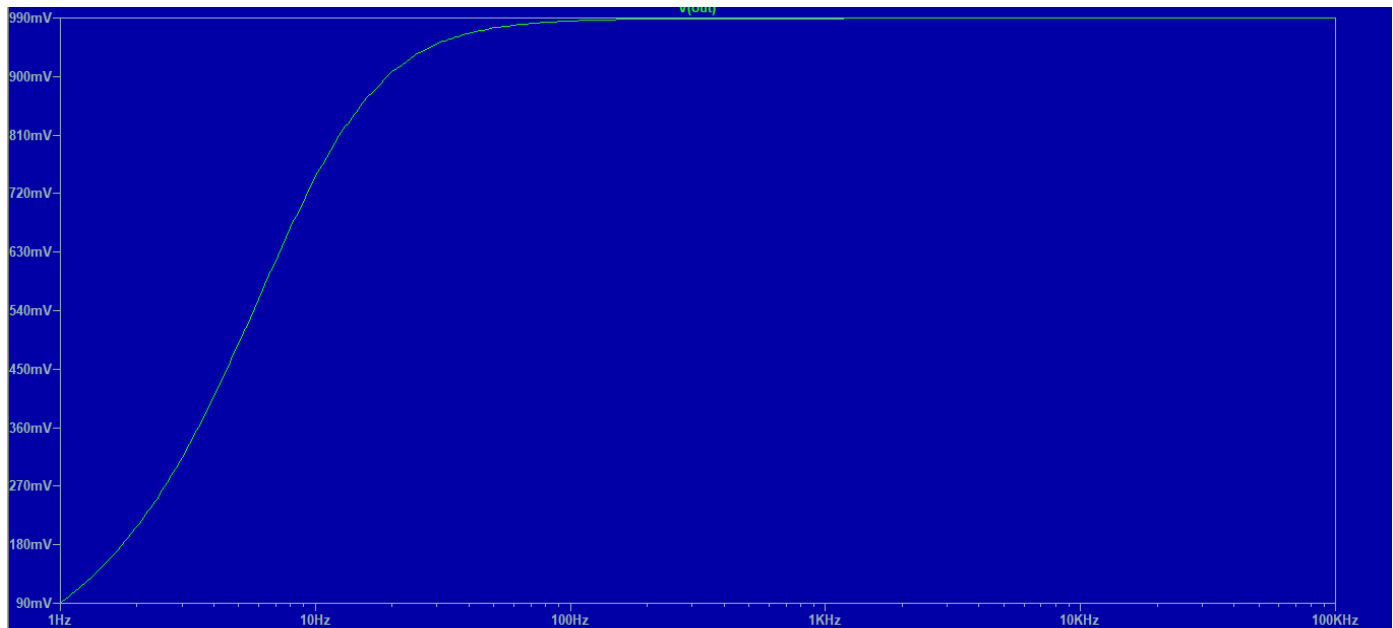

$$U_{-3dB} = 990mV / \sqrt{2} = 0.7000357134V$$

$$f_{-3dB} = 8.8100034 \text{ Hz}$$

DC values of U_b , U_k , U_e , I_b , I_k , I_e :

U_b : 9.85723 V I_b : 75.5218 μ A

U_k : 15.458555 V I_k : 22.7072 mA

U_e : 9.1130911 V I_e : -22.7828 mA

vrms: $\text{RMS}(v(\text{out})) = \underline{2.4958}$ FROM 0 TO 0.003

P_{out} is output signal power

$$P_{out} = u_{out}^2 / R_a = (\underline{2.4958})^2 / 200 = \underline{0.0311450882 \text{ W}}$$

P_{DC} is DC power from supply

$$I_{DC} \sim I_e \text{ (average value)}$$

$$P_{DC} = U_{DC} \cdot I_{DC} = 20 \cdot 22.7828 \times 10^{-3} \\ = \underline{0.455656 \text{ W}}$$

$$\text{Power Gain} = P_{out} / P_{in} = \\ 0.0311450882 / 0.0091530024 = \underline{3.4027182381 \text{ W}}$$

$$P_{in} = P_{in \text{ RMS}} = V_{in \text{ rms}} \cdot I_{in \text{ rms}} = \\ 2.8272359327 \text{ V} \cdot 1.618719238 \times 10^{-3} \text{ A} = \\ \underline{4.5765011946 \times 10^{-3} \text{ W}}$$

R_{out} – amplifier output resistance

$$R_{out} = R_3 \left((u_{out1} / u_{out}) - 1 \right)$$

$$u_{out1} = 3.9719388 \text{ V} / \sqrt{2} = \underline{2.8085848599 \text{ V}}$$


$$u_{out} = 3.4422098 \text{ V} / \sqrt{2} = \underline{2.4340093262 \text{ V}}$$

$$R_{out} = 200 \cdot ((2.8085848599 / 2.4340093262) - 1) \\ = \underline{30.77847974 \Omega}$$


$$\text{power loss } \Delta P = P_{DC} - P_{out} \\ = 0.455656 - 0.0311450882 = \underline{0.4245109118 \text{ W}}$$

$$\eta = P_{out} / P_{DC} = \underline{0.068352196}$$


Class B Power Amplifier

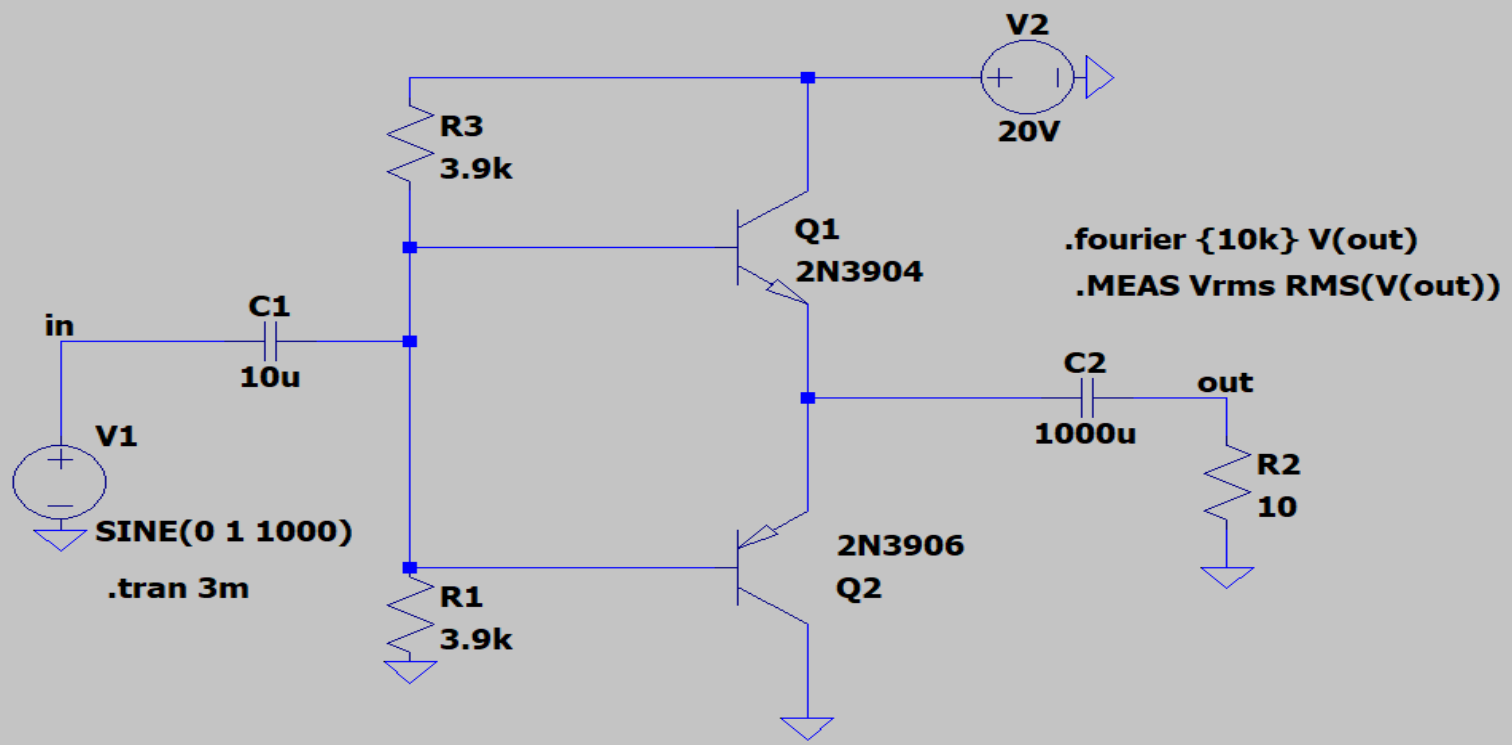

Transient response

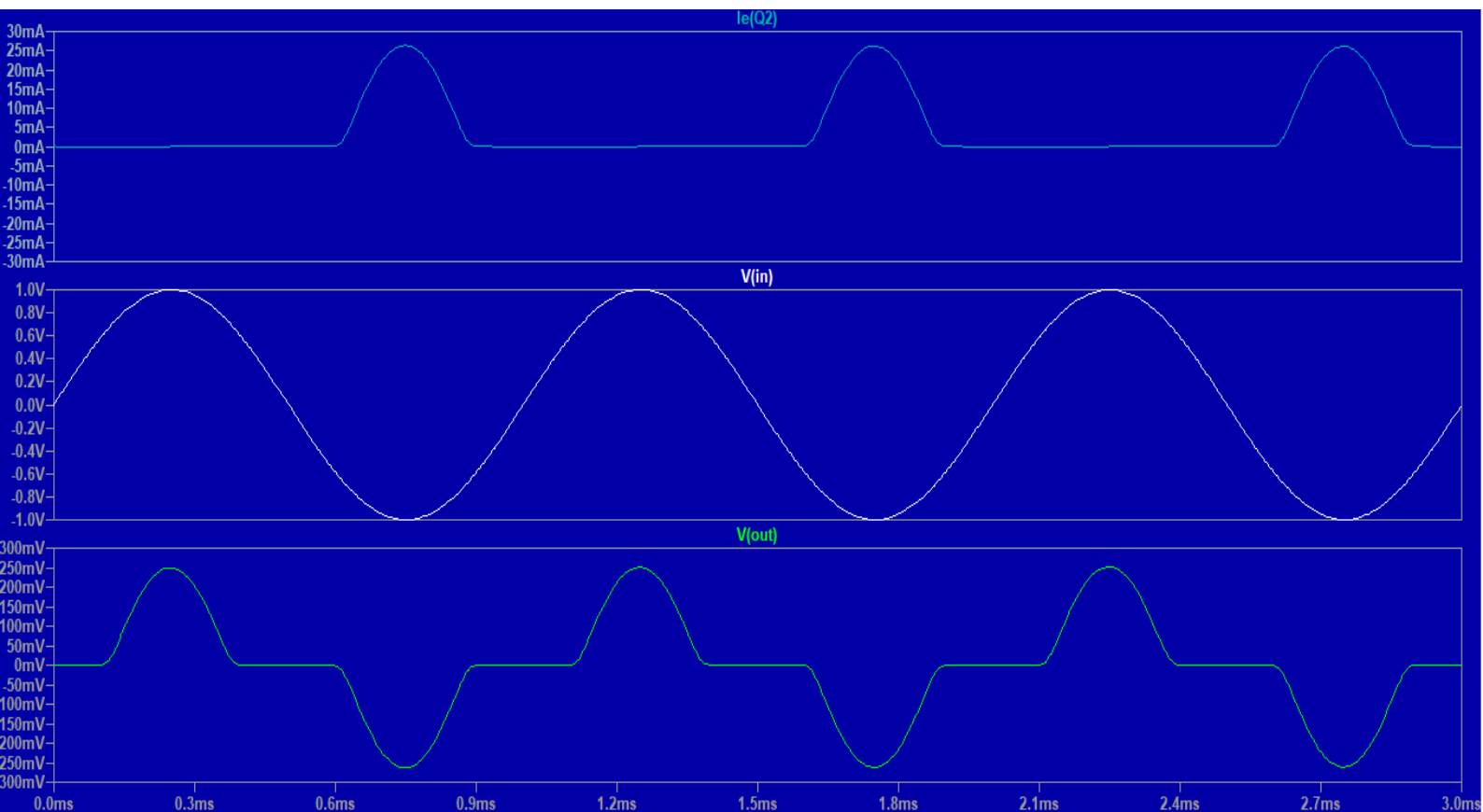

AC Response and Bandwith (-3dB)

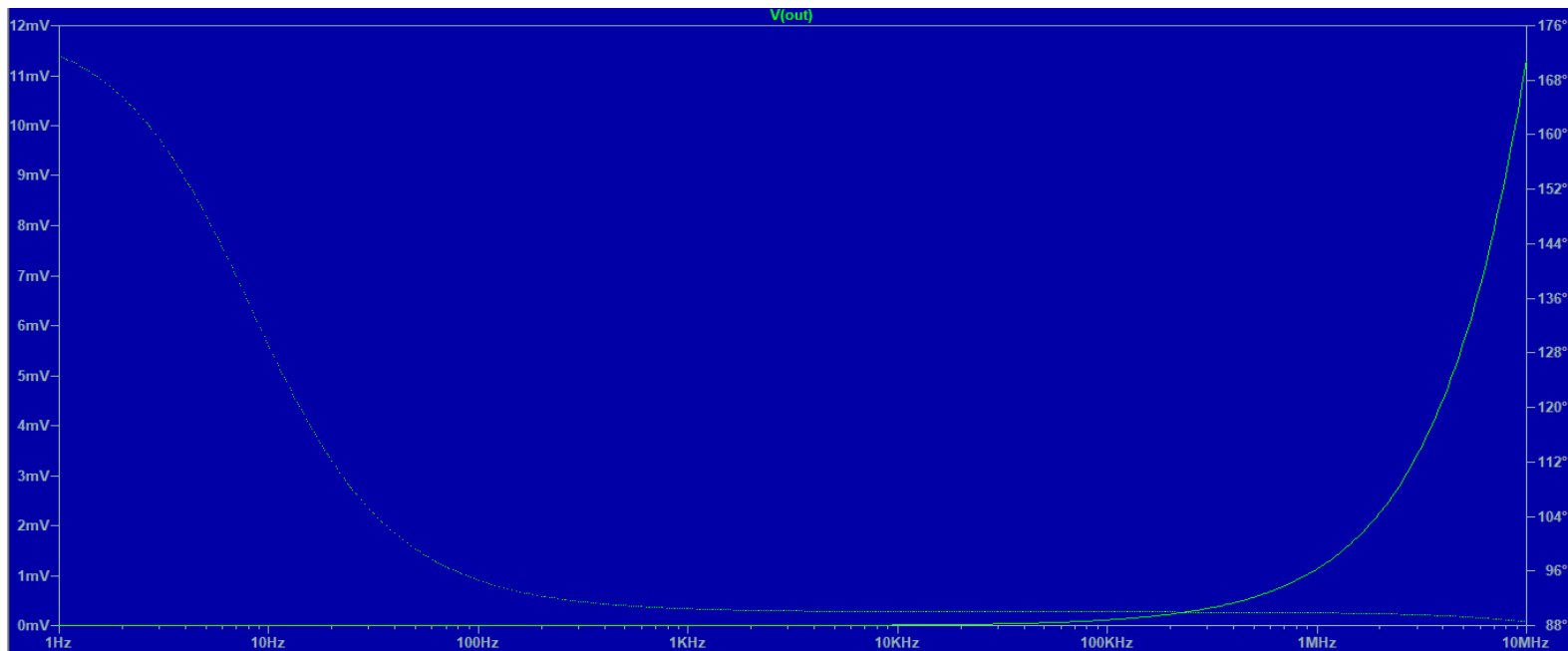

$$U_{-3dB} = 11.305323\text{mV} / \sqrt{2} = 7.9940705568 \text{ mV}$$

$$f_{-3dB} = 7.0421207\text{MHz}$$

DC values of U_b , U_k , U_e , I_b , I_k , I_e :

U_b : 10 V I_b : 10 pA

U_k : 20 V I_k : 10.08 pA

U_e : 9.9979 V I_e : -10.02499 pA

vrms: RMS (v(out))=0.00652789 FROM 1 TO 1e+07

P_{out} is output signal power

$$P_{out} = u_{out}^2 / R_a = (0.00652789)^2 / 10 = \underline{0.0000042613 \text{ W}}$$

P_{DC} is DC power from supply

$$(P_{DC} = U_{DC} \cdot I_{DC}) \quad I_{DC} \sim 1/\pi * I_{ep}$$

(I_{ep} is peak value of Q1 emitter or Q2 emitter)

$$I_{ep} = 0.0317516413 \text{ pA}$$

$$P_{DC} = U_{DC} \cdot I_{DC} = 20 \cdot 0.0317516413 = \\ = \underline{0.6350328626 \text{ pW}}$$

$$\text{Power Gain} = P_{out} / P_{in} = \underline{4.26100000E-16 \text{ W}}$$

$$P_{in} = P_{in \text{ RMS}} = V_{in \text{ rms}} \cdot I_{in \text{ rms}} = 1 \times 10^{-10}$$

$$\underline{0.1772870496 \text{ V} \cdot 644.27349 \times 10^{-12} \text{ A} = 1 \times 10^{-10}}$$

1. R_{out} – amplifier output resistance

$$R_{out} = R_3 \cdot ((u_{out1} / u_{out}) - 1)$$

$$u_{out1} = 0.7076175951 \text{ V} \quad u_{out} = 0.1772870496 \text{ V}$$

$$R_{out} = 29.914223639 \text{ } \Omega$$

$$\text{power loss } \Delta P = P_{DC} - P_{out} =$$

$$0.6350328626 \text{ pW} - 0.0000042613 \text{ W} = \underline{- 0.0000042613 \text{ W}}$$

$$\eta = P_{out} / P_{DC} = \underline{6.71036139E-21}$$

Circuit: * C:\Users\templ\OneDrive\Masaüstü\labwork 3\Draft1.asc

Direct Newton iteration for .op point succeeded.

N-Period=1

Fourier components of V(out)

DC component:-3.55417e-05

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+4	7.019e-5	1.000e+0
2	2.000e+4	6.257e-5	8.915e-1
3	3.000e+4	5.385e-5	7.672e-1
4	4.000e+4	4.601e-5	6.555e-1
5	5.000e+4	3.957e-5	5.638e-1
6	6.000e+4	3.444e-5	4.907e-1
7	7.000e+4	3.034e-5	4.323e-1
8	8.000e+4	2.704e-5	3.852e-1
9	9.000e+4	2.434e-5	3.468e-1

Total Harmonic Distortion: 168.141291%(198.278953%)


vrms: RMS(v(out))=0.132291 FROM 0 TO 0.003|

Date: Wed May 6 21:02:54 2020


Total elapsed time: 0.144 seconds.

tnom = 27


Class AB Amplifier

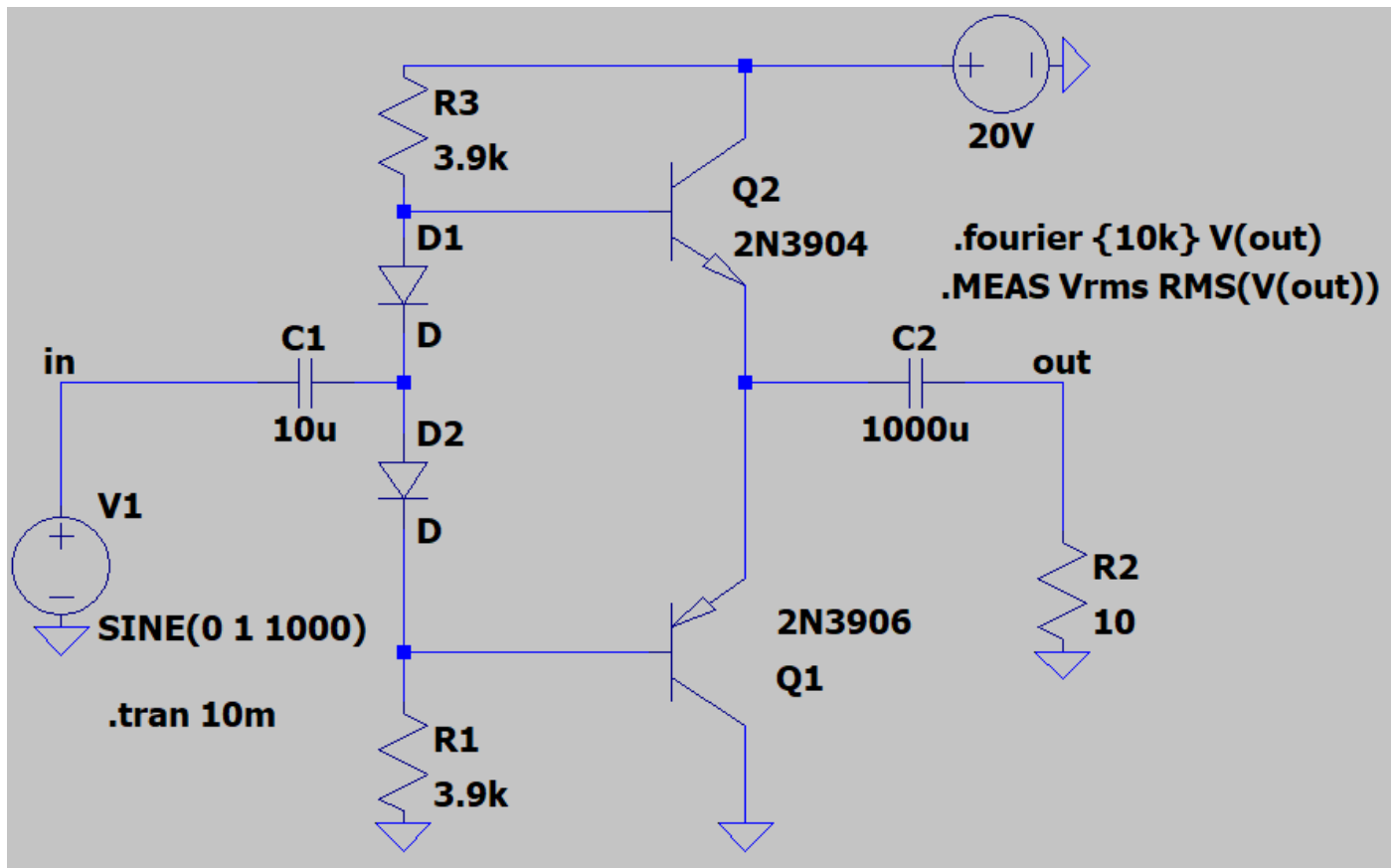

Transient response of AB power amplifier

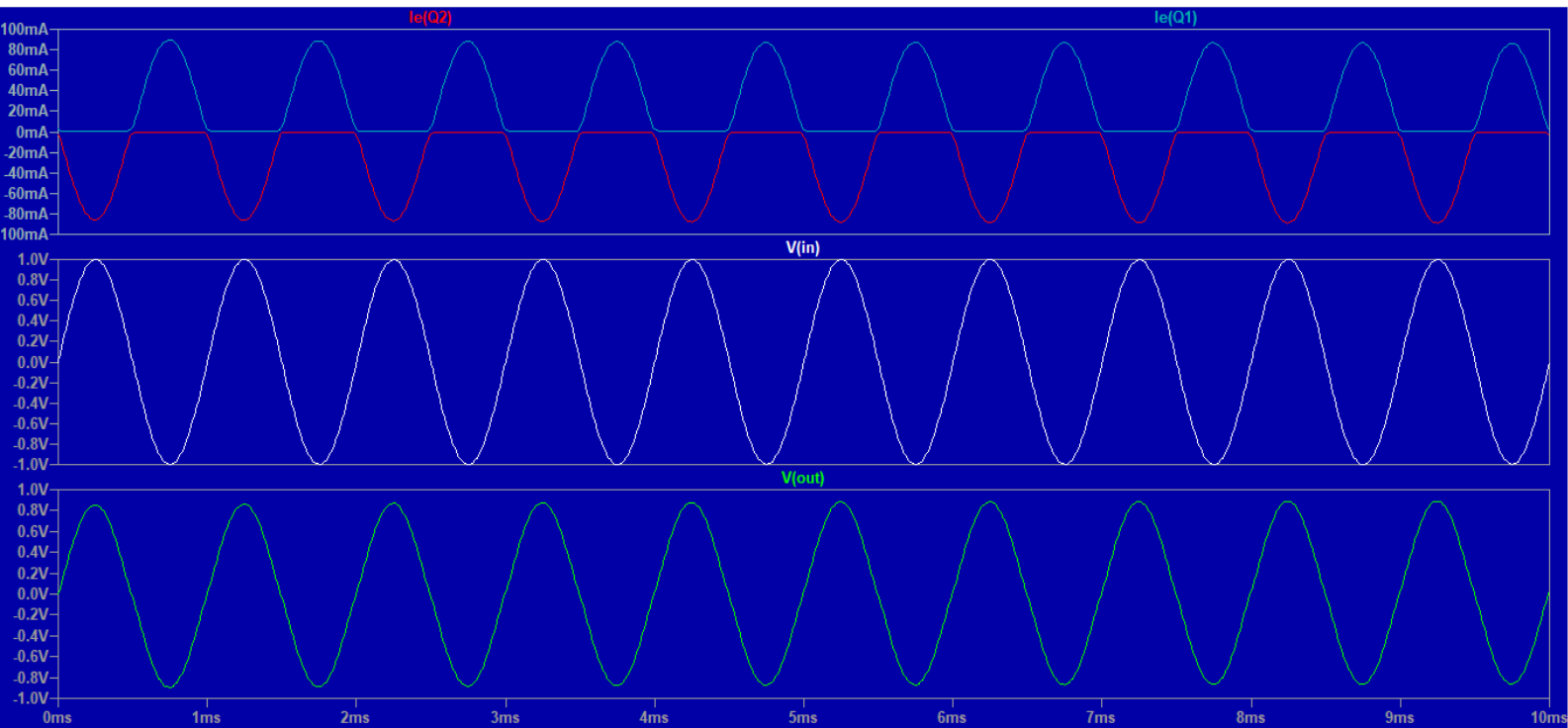


AC Response and Bandwidth

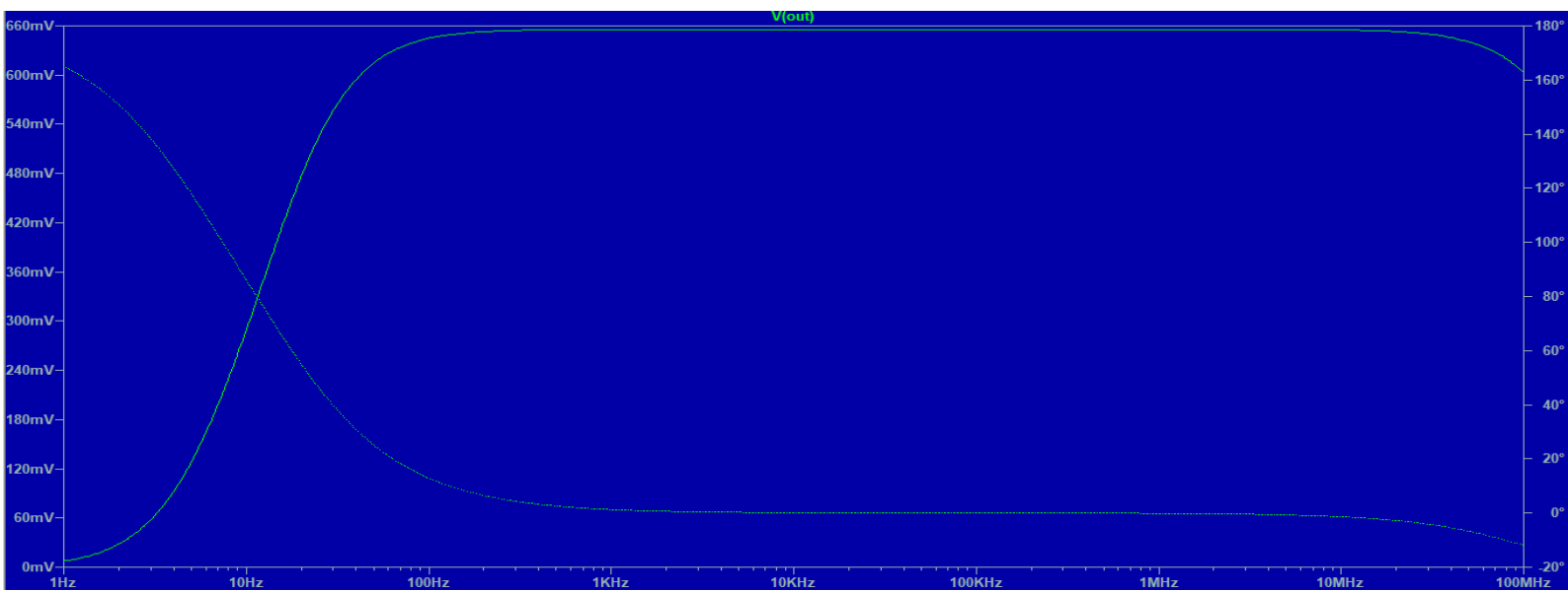

$$U_{-3dB} = 0.4666904756 \text{ V}$$

$$f_{-3db} = 19.276997\text{Hz}$$

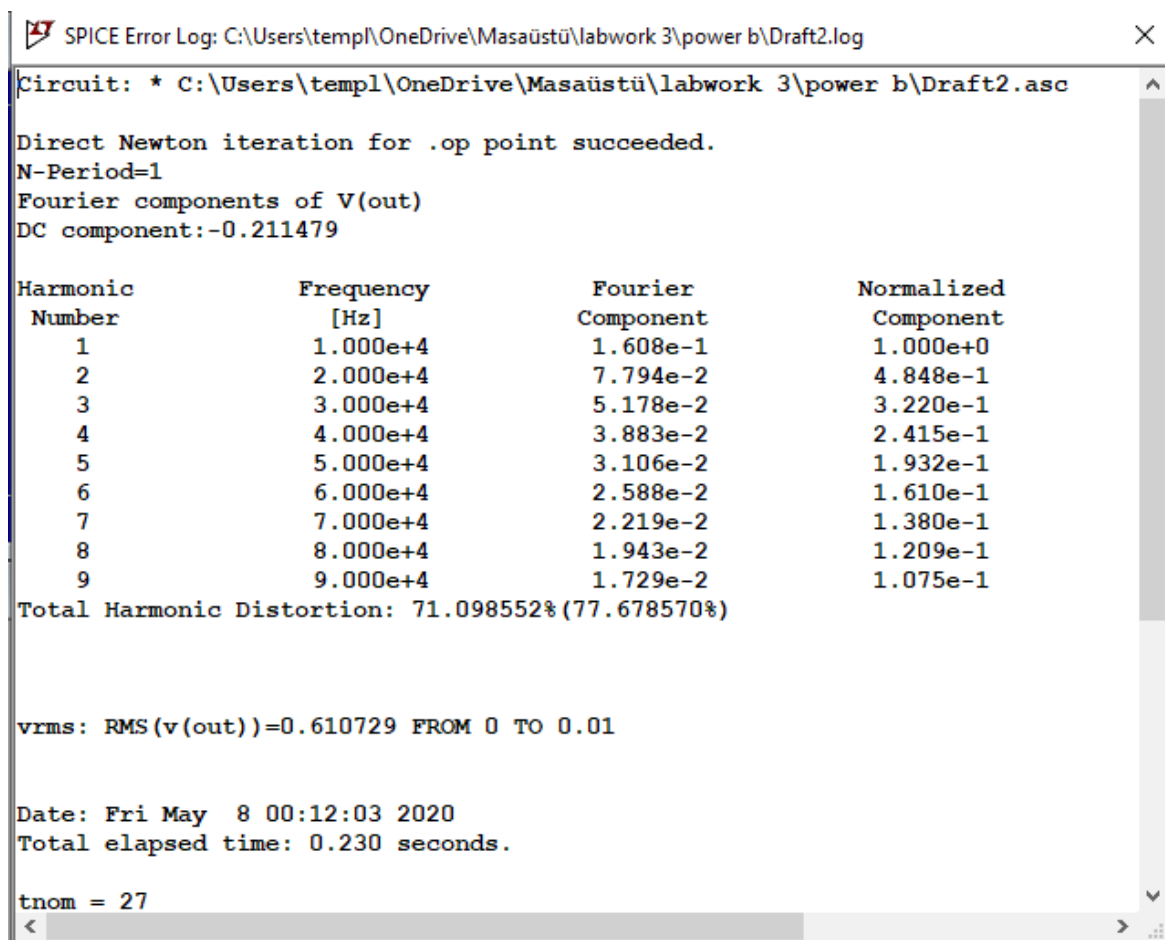

DC values of $U_b, U_k, U_e, I_b, I_k, I_e$:

U_b : 10 V I_b : 10 pA

U_k : 20 V I_k : 10.08 pA

U_e : 9.9979 V I_e : 17.76 fA

vrms: RMS(v(out))=0.636995 FROM 1 TO 1e+08

P_{out} is output signal power

$$P_{out} = u_{out}^2 / R_a = (0.636995)^2 / 10 = 0.040576263 \text{ W}$$

P_{DC} is DC power from supply

$$(P_{DC} = U_{DC} \cdot I_{DC}) \quad I_{DC} \sim 1/\pi \cdot I_{ep}$$

(I_{ep} is peak value of Q1 emitter or Q2 emitter)

$$I_{ep} = 89.348271 \text{ mA}$$

$$P_{DC} = U_{DC} \cdot I_{DC} = 20 \cdot 0.0351612025 = \underline{0.70322405 \text{ W}}$$

$$\text{Power Gain} = P_{out} / P_{in} = 0.040576263 / 5 \times 10^{-10} \\ = \underline{8.11525300 \text{E-}13}$$

$$P_{in} = P_{in \text{ RMS}} = V_{in \text{ rms}} \cdot I_{in \text{ rms}} \\ = 0.7059449482 \cdot 7 \times 10^{-10} = \underline{5 \times 10^{-10}}$$

2. R_{out} – amplifier output resistance

$$R_{out} = R_3 \cdot ((u_{out1} / u_{out}) - 1)$$

$$u_{out1} = 709.4682425499 \text{ mV}$$

$$u_{out} = 620.8701948287 \text{ mV}$$

$$R_{out} = \underline{1.426997921 \Omega}$$

$$\text{power loss } \Delta P = P_{DC} - P_{out} =$$

$$0.70322405 - 0.040576263 = \underline{0.662647787 \text{ W}}$$

$$\eta = P_{out} / P_{DC} = 0.040576263 / 0.70322405 = \underline{0.0577003346}$$

Conclusion

At the end of the experiment, the result that I acquired is not accurate to the theory also values of the efficiency and power gain are not satisfying because of their low values. The efficiency of Class A amplifier expected to be lowest but in this situation it was the highest so its not accurate to the theory also the Class AB Amplifier suppose to be higher than Class A amplifier and lower than Class B amplifier but in this condition its the lowest amplifier. When it comes to power gain Class A amplifier has the highest value and Class AB amplifiers follows it and Class B amplifier has the lowest power gain value which is also not accurate to the theory